


# CLASSROOM PRACTICE TEST-02

## NETWORK THEORY (SOLUTIONS)

### ANSWER KEY

<b>1</b>	(a)	<b>14</b>	(b)	<b>27</b>	(a)	<b>40</b>	(a)	<b>53</b>	(b)
<b>2</b>	(a)	<b>15</b>	(b)	<b>28</b>	(b)	<b>41</b>	(b)	<b>54</b>	(a)
<b>3</b>	(b)	<b>16</b>	(d)	<b>29</b>	(c)	<b>42</b>	(a)	<b>55</b>	(a)
<b>4</b>	(b)	<b>17</b>	(a)	<b>30</b>	(c)	<b>43</b>	(c)	<b>56</b>	(a)
<b>5</b>	(c)	<b>18</b>	(a)	<b>31</b>	(d)	<b>44</b>	(b)	<b>57</b>	(c)
<b>6</b>	(d)	<b>19</b>	(b)	<b>32</b>	(b)	<b>45</b>	(c)	<b>58</b>	(a)
<b>7</b>	(b)	<b>20</b>	(c)	<b>33</b>	(d)	<b>46</b>	(d)	<b>59</b>	(c)
<b>8</b>	(c)	<b>21</b>	(d)	<b>34</b>	(a)	<b>47</b>	(a)	<b>60</b>	(c)
<b>9</b>	(b)	<b>22</b>	(b)	<b>35</b>	(d)	<b>48</b>	(d)	<b>61</b>	(d)
<b>10</b>	(d)	<b>23</b>	(c)	<b>36</b>	(b)	<b>49</b>	(c)	<b>62</b>	(a)
<b>11</b>	(d)	<b>24</b>	(b)	<b>37</b>	(a)	<b>50</b>	(d)	<b>63</b>	(b)
<b>12</b>	(b)	<b>25</b>	(c)	<b>38</b>	(c)	<b>51</b>	(a)	<b>64</b>	(b)
<b>13</b>	(c)	<b>26</b>	(a)	<b>39</b>	(a)	<b>52</b>	(d)	<b>65</b>	(c)

1. (a)

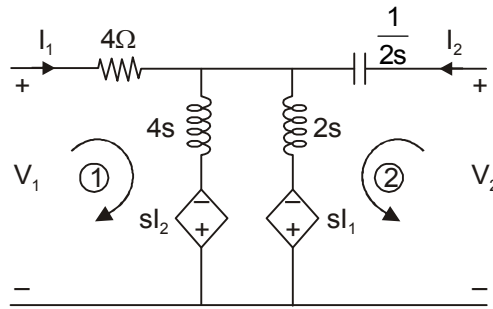

Loop-1 :

$$-V_1 + (4 + 4s)I_1 - sI_2 = 0$$

$$V_1 = (4 + 4s)I_1 - sI_2$$

Loop-2 :

$$-V_2 + \left(2s + \frac{1}{2s}\right)I_2 - sI_1 = 0$$

$$V_2 = -sI_1 + \left(2s + \frac{1}{2s}\right)I_2$$

From (1) and (2)


$$Z = \begin{bmatrix} (4 + 4s) & -s \\ -s & 2s + \frac{1}{2s} \end{bmatrix}$$

2. (a)

$$L = L_1 + L_2 - 2M$$

$$X_L = X_1 + X_2 - 2X_m$$

$$X_L = 2 + 6 - 2 \times 3 = 2\Omega$$

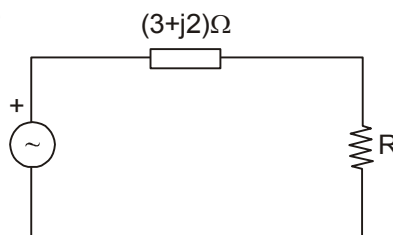

For maximum power transfer,

$$R = |3 + j2|$$

$$R = 3.6\Omega$$

3. (b)

Applying superposition theorem, it is known that if all current source value are doubled, then node voltages also are doubled.

4. (b)

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

∴ when C increases,  $\omega_0$  will decrease.

$$\text{Bandwidth} = \frac{R}{L} = \text{thus constant}$$

5. (c)

The  $\Delta$ -connected impedance can be replaced by Y connected impedance using

$$Z_Y = \frac{Z_\Delta}{3}$$

$$\begin{aligned} Z_Y &= \frac{15}{3} \\ &= 5\Omega \end{aligned}$$

6. (d)


Conditions for two port reciprocal network,

Parameter	Condition
Z	$Z_{12} = Z_{21}$
Y	$Y_{12} = Y_{21}$
h	$h_{12} = -h_{21}$
ABCD	$AD - BC = 1$

7. (b)

The above problem will be solved by the use of superposition principle.


Disabling  $i_b$

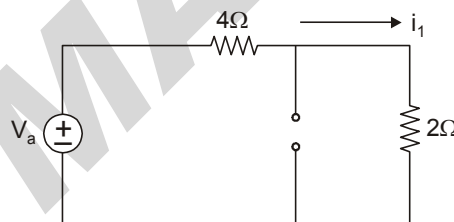

$$i_1 = \frac{v_a}{4+2} = \frac{10\sqrt{2}}{6} \cos t$$

$$= 1.67\sqrt{2} \cos t$$

Disabling  $V_a$

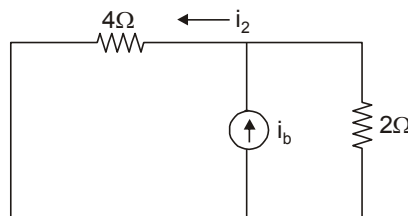

$$i_2 = i_b \left( \frac{2}{2+4} \right)$$

$$= \frac{10\sqrt{2} \cos 2t}{3} = 3.33\sqrt{2} \cos 2t$$

$\therefore$  Total current through  $4\Omega$  resistor.

$$i = i_1 - i_2$$

$$= 1.67\sqrt{2}\cos t - 3.33\sqrt{2}\cos 2t$$


$$\therefore R_{\text{ms}} \text{ current through resistor} \quad I = \sqrt{(1.67)^2 + (3.33)^2}$$

$$= 3.72 \text{ A}$$

$$\therefore \text{Power loss in resistor} = I^2 R = (3.72)^2 \times 4$$

$$= 55.5 \text{ W}$$

8. (c)

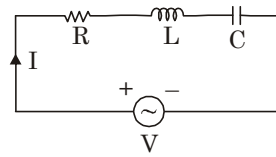

Total impedance of RLC series circuit is

$$Z = R + j(X_L - X_C)$$

at resonance

$$X_L = X_C$$

 $\therefore$ 

$$Z = R$$

 $\therefore$ 


$$X_L = X_C$$

$$I X_L = I X_C$$

 $\Rightarrow$ 

$$jI\omega L = \frac{I}{j\omega C}$$

$$|V_L| = |V_C|$$

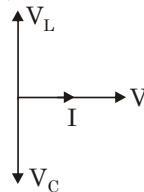At resonance, RLC series circuit voltage across L and C have equal magnitude but  $180^\circ$  out of phase from each other.

9. (b)

Transients and linearity is not dependent. A circuit which is linear may have transients. Transients are there when energy storage element like inductor and capacitor are present, both are linear.

10. (d)

Transmission Parameters Network 'b'

$$= \begin{bmatrix} 1 & a \\ 3 & 2 \end{bmatrix} \begin{bmatrix} 1 & a \\ 3 & 2 \end{bmatrix} = \begin{bmatrix} 1+3a & 3a \\ 9 & 3a+4 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

For reciprocity,  $[AD - BC] = 1$ 


$$(3a+4)(1+3a) - (3a) \times 9 = 1$$

$$9a^2 - 12a + 4 = 1$$

$$a = 1 \text{ or } 1/3$$

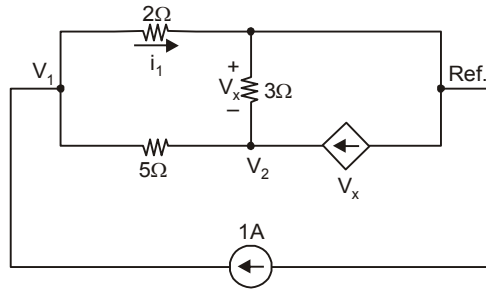11. (d)

Selecting the rightmost node as reference node, and leftmost node as  $V_1$



Now, by nodal analysis

$$\frac{V_1 - V_2}{5} + \frac{V_1}{2} = 1$$

$$7V_1 - 2V_2 = 10 \quad \dots(1)$$

and  $\frac{V_2}{3} + \frac{V_2 - V_1}{5} = V_x$

Since,  $V_x = -V_2$

$$\therefore \frac{V_2}{3} + \frac{V_2 - V_1}{5} = -V_2$$

$$\text{or } -3V_1 + 23V_2 = 0 \quad \dots(2)$$

[eqn. (1)  $\times$  3] + [eqn. (2)  $\times$  7] gives

$$155V_2 = 30$$

or  $V_2 = 0.1935\text{V}$


$\therefore V_1 = 1.4839\text{ V}$

$$i_1 = \frac{V_1}{2} = \frac{1.4839}{2} = 0.7419\text{A}$$

or  $i_1 = 742\text{ mA}$

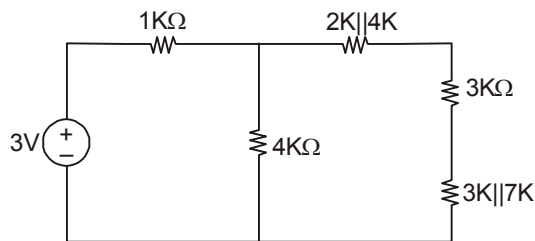12. (b)


By resistor combinations, the circuit can be simplified as



$$2\text{K}\Omega \parallel 4\text{K}\Omega = \frac{2 \times 4}{2 + 4} = \frac{8}{6} = \frac{4}{3}\text{K}\Omega$$

$$3\text{K}\Omega \parallel 7\text{K}\Omega = \frac{3 \times 7}{3 + 7} = \frac{21}{10}\text{K}\Omega$$

Further

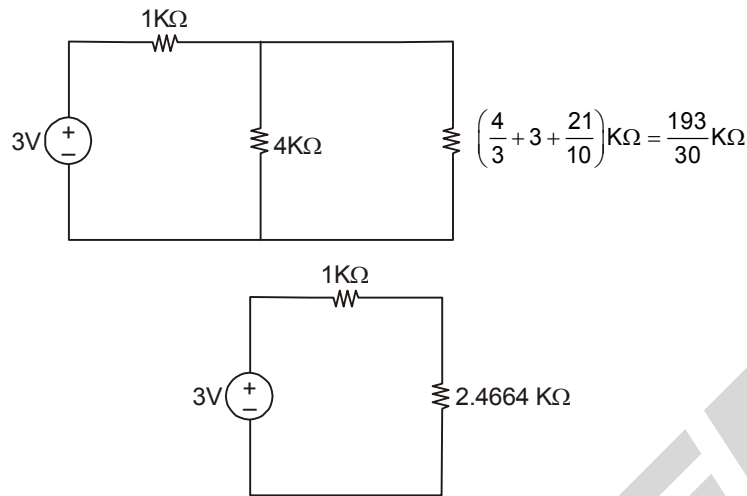

Voltage across 4KΩ resistor

$$V_{4\Omega} = 3 \times \left( \frac{2.4664}{2.4664 + 1} \right) = 2.1345 \text{ V}$$

$$|V_x| = \text{Voltage across } (3k \parallel 7k)$$

$$\text{Thus, } |V_x| = (2.1345) \times \frac{\left(\frac{21}{10}\right)}{\left(\frac{4}{3} + 3 + \frac{21}{10}\right)} = 0.6968 \text{ v}$$

OR  $V_x = 0.697\text{V}$

13. (c)

Let,  $P_1$  = Power supplied by 2 sin(2t) A source

$P_2$  = Power supplied by 4 cos(4t) A source

$P_3$  = Power supplied by 4 sin(2t) A source

So, total power consumed by resistance

$$P = P_1 + P_2 + P_3 \quad \dots(i)$$

$$= (I_{1\text{rms}})^2 R + (I_{2\text{rms}})^2 R + (I_{3\text{rms}})^2 R$$

$$P = \left(\frac{2}{\sqrt{2}}\right)^2 \times 2 + \left(\frac{4}{\sqrt{2}}\right)^2 \times 2 + \left(\frac{4}{\sqrt{2}}\right)^2 \times 2$$

$$P = 36\text{W} \quad (\text{answer is wrong})$$

Note: I

$P = P_1 + P_2 + P_3$  is not valid because 2 sin(2t) and 4 sin(2t) are same frequency terms so first they should be added together and then power consumed should be calculated.

$$i_{(t)} = 6 \sin 2t + 4 \cos 4t$$

$$P = P_1 + P_2$$

∴

$P_1$  = Power supplied by 6 sin2t A

$P_2$  = Power supplied by 4 cos4t A

So,

$$\begin{aligned}
 P &= (I_{1\text{rms}})^2 R + (I_{2\text{rms}})^2 R \\
 &= \left(\frac{6}{\sqrt{2}}\right)^2 \times 2 + \left(\frac{4}{\sqrt{2}}\right)^2 \times 2 \\
 P &= 52\text{W}
 \end{aligned}$$


**Note : II**

Here superposition of power is valid  $P = P_1 + P_2$

because two sinusoidal sources of different frequency are acting on a network.

**14. (b)**

By nodal analysis

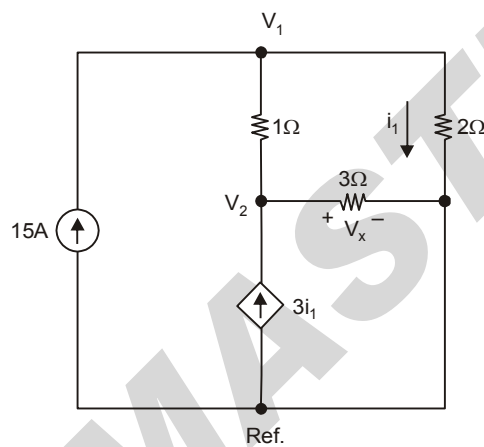

At node 1,

$$\frac{V_1 - V_2}{1} + \frac{V_1}{2} = 15$$

$$\text{or } 3V_1 - 2V_2 = 30 \quad \dots(1)$$

At node 2

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} = 3i_1$$

$$\text{Where, } i_1 = \frac{V_1}{2}$$

$$\text{So, } V_2 - V_1 + \frac{V_2}{3} = \frac{3V_1}{2}$$

$$\text{So, } -15V_1 + 8V_2 = 0 \quad \dots(2)$$

[eq. (1)  $\times$  5] + eq. (2), gives

$$-2V_2 = 150$$

$$\text{or, } V_2 = -75$$

$$\therefore V_1 = -40\text{ V}$$

Power supplied by dependent source is

$$P = \frac{3V_1}{2} \times V_2 = (-60)(-75) = 4500 \text{ W}$$


or  $P = 4.5 \text{ kW}$

15. (b)

Using super position theorem.

**For 1V source**, let current through  $2\Omega$  is  $I_1$

by short circuiting 2V source and open circuiting current source. the equivalent circuit is:

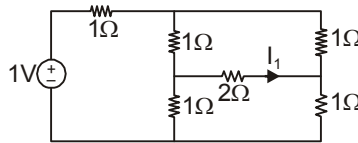


(Fig. 1)

$I_1 = 0\text{A}$  because the bridge made by  $1\Omega$  is balanced.

**for 1A source**

By short circuiting the 2V and 1V source, let current flow through  $2\Omega$  is  $I_2$

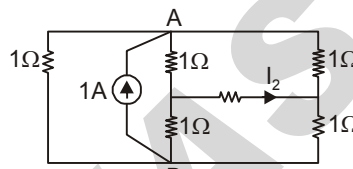


(Fig.2)


Using current to voltage source transformation the equivalent circuit will be same as fig.(1) so  $I_2 = 0\text{A}$ .

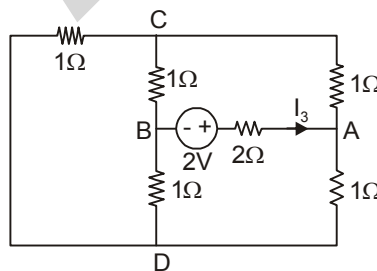**for 2V ;**

short circuiting 1V source and by open circuiting 1A current sources the equivalent circuit is




redrawing this as

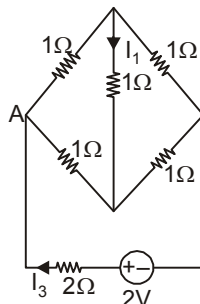

$I_1 = 0$  (because bridge is balanced)



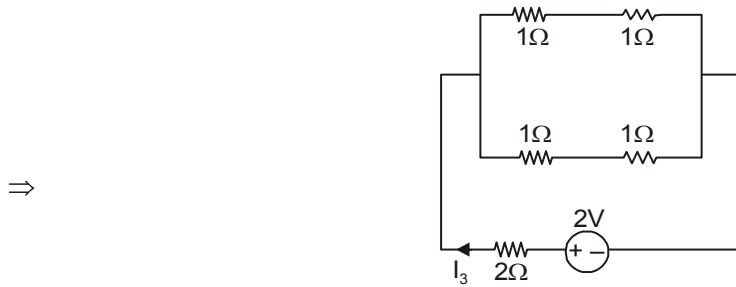

$$R_{eq} = 3\Omega$$

$$I_3 = \frac{2}{3} \text{ Amp.}$$

So,


$$I = I_1 + I_2 + I_3 = 0 + 0 + \frac{2}{3}$$

$$I = \frac{2}{3} \text{ Amp.}$$

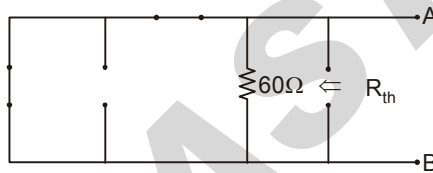16. (d)


For  $R_{th}$ ,

Short circuiting the voltage sources and open circuiting the current sources.



$$R_{th} = 60\Omega$$

For  $V_{th}$ ,

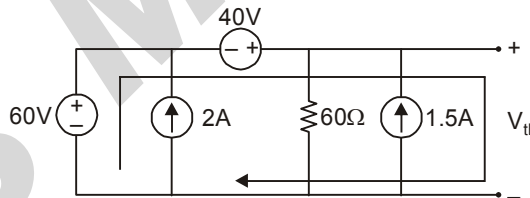

Using KVL equation in loop

$$-60 - 40 + V_{th} = 0$$

⇒

$$V_{th} = 100 \text{ V}$$


So,

$$I_{sc} = \frac{V_{th}}{R_{th}} = \frac{100}{0} = \infty$$

⇒ Norton equivalent circuit does not exist.

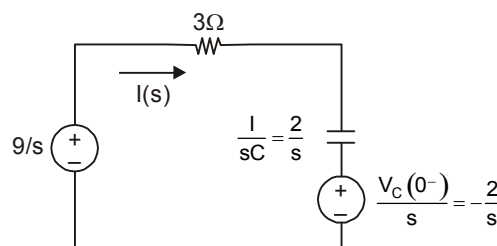17. (a)

By drawing frequency-domain equivalent circuit



By KVL

$$\frac{9}{s} = 3I(s) + \frac{2I(s)}{s} - \frac{2}{s}$$

or 
$$I(s) = \frac{11}{3} \left( \frac{1}{s + \frac{2}{3}} \right)$$

or 
$$i(t) = \frac{11}{3} e^{(-2/3)t}$$

Now, 
$$V_c(t) = \frac{1}{C_0} \int_0^t i(t) dt - 2$$

$$= \frac{22}{3} \times \left( -\frac{3}{2} e^{(-2/3)t} \right) \Big|_0^t - 2$$

$$= -11e^{(-2/3)t} + 9$$

$$\therefore V_c(t) = [9 - 11e^{(-2/3)t}] u(t)$$

18. (a)

$$Q_0 = 300 \mu\text{C} \text{ at } 6 \mu\text{F} \text{ capacitor}$$

$$\therefore Q_0 = CV_0$$

$$V_0 = \frac{Q_0}{C} = \frac{300}{6} = 50\text{V}$$

The two parallel capacitors have an equivalent capacitance of  $3 \mu\text{F}$ . Then this capacitor is in series with  $6 \mu\text{F}$ .

Time constant, 
$$\tau = RC_{eq} = 20 \times \left( \frac{3 \times 6}{3 + 6} \right) = 40$$

At,  $t = 0^+$

KVL gives 
$$V_R = \frac{300}{6} = 50\text{V}$$


and at  $t = \infty$  capacitor behave open circuit

so 
$$V_R \rightarrow 0$$

$$\Rightarrow V_R = 50 e^{-t/40}\text{V}$$

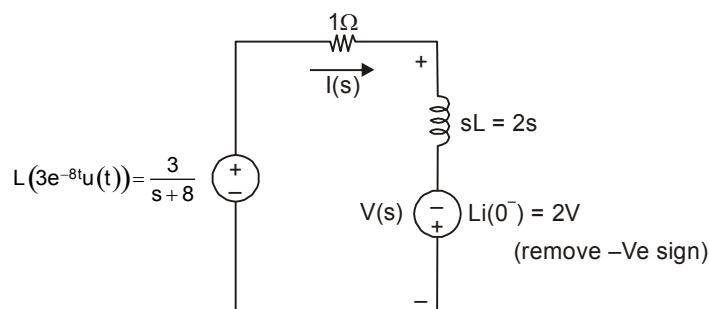19. (b)

By drawing equivalent frequency-domain circuit including the initial current in the inductor.



$$I(s) = \frac{\frac{3}{s+8} + 2}{1+2s} = \frac{s+9.5}{(s+8)(s+0.5)}$$

and  $V(s) = 2sI(s) - 2$

Thus, 
$$V(s) = \frac{2s(s+9.5)}{(s+8)(s+0.5)} - 2$$

$$= \frac{2s-8}{(s+8)(s+0.5)} = \frac{A}{s+8} + \frac{B}{s+0.5}$$

$$A = \left( \frac{2s-8}{s+0.5} \right)_{s=-8} = 3.2$$

$$B = \left( \frac{2s-8}{s+8} \right)_{s=-0.5} = -1.2$$

Thus, 
$$V(s) = \frac{3.2}{s+8} - \frac{1.2}{s+0.5}$$

Taking inverse (Laplace transform)

$$V(t) = [3.2e^{-8t} - 1.2e^{-0.5t}]u(t)$$

20. (c)

$$V_C = V_0 e^{-t/\tau} \quad \text{[discharging of capacitor]}$$

At  $t = t_1$ ,  $V_C = V_1$

$$V_1 = V_0 e^{-t_1/\tau} \quad \dots(i)$$

At  $t = t_2$ ,  $V_C = V_2$

$$V_2 = V_0 e^{-t_2/\tau} \quad \dots(ii)$$

equation (i) / (ii)

$$\frac{V_1}{V_2} = \frac{e^{-t_1/\tau}}{e^{-t_2/\tau}}$$


$$\Rightarrow \frac{V_1}{V_2} = e^{\frac{[t_1-t_2]}{\tau}}$$

$$\Rightarrow \left( \ln \frac{V_1}{V_2} \right) = \frac{t_2 - t_1}{\tau}$$

$$\Rightarrow \tau = \frac{t_2 - t_1}{\ln V_1 - \ln V_2}$$

21. (d)

In s-domain

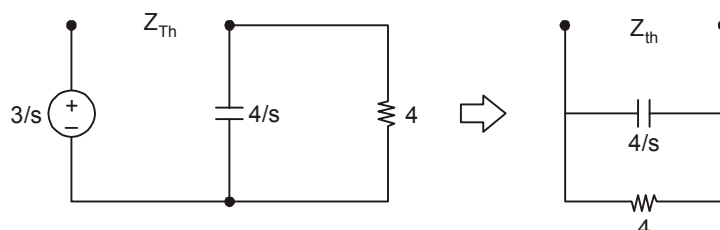


$$Z_{Th} = \frac{4}{s} \parallel 4$$

$$= \frac{\frac{4}{s} \times 4}{\frac{4}{s} + 4}$$

$$Z_{Th} = \frac{4}{s+1}$$

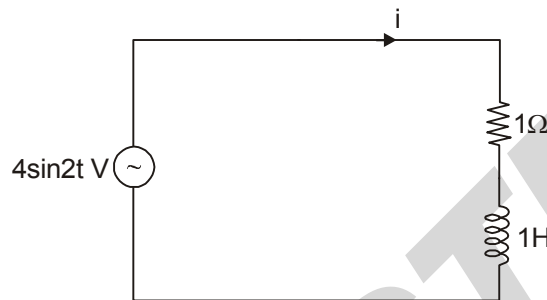22. (b)

$s \rightarrow 1$  for long time i.e., steady state



$$V_s = 4 \sin 2t; \omega = 2$$

$$\bar{V}_s = 2\sqrt{2} \angle 0^\circ$$

$$\bar{Z} = 1 + j2 = 2.24 \angle 63.4^\circ \Omega$$

$$\bar{I} = \frac{\bar{V}_s}{\bar{Z}} = \frac{2.83}{2.24} \angle -63.4^\circ \text{ Amp}$$


$$i(t) = 1.26\sqrt{2} \sin(2t - 63.4^\circ)$$

$$i(t) = 1.78 \sin(2t - 63.4^\circ) \text{ Amp}$$

$s \rightarrow 1$  for long time,

$$V_s(t) = 4 \sin 2t \text{ Volt}$$
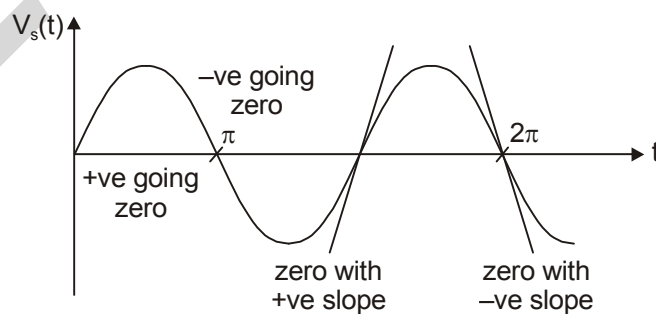
$$i(t) = 1.78 \sin(2t - 63.4^\circ) \text{ Amp}$$



$$V_s(t) = V_m \sin \omega t = V_m \sin \theta$$


$$V_s = 0 \Rightarrow \theta = 0, \pi \text{ (zero with -ve slope)}$$

$$\text{So, } V_s(t) = \sin 2t \Rightarrow 2t = \pi, t = \frac{\pi}{2}$$

$$\text{So, at } 2t = \pi; \quad i(t) = 1.78 \sin(2t - 63.4^\circ)$$

$$i(t) = 1.78 \sin(\pi - 63.4^\circ)$$

$$i(t) = 1.59 \text{ Amp}$$

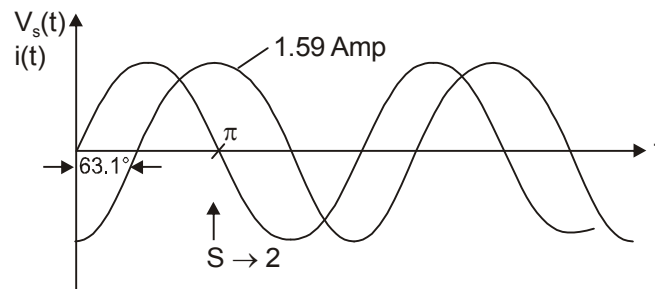


At the instance,  $S \rightarrow 2$  inductor current,  $i = 1.59$  Amp.

$$S \rightarrow 2, t = 0$$

$$i(0^-) = 1.59 \text{ Amp}$$

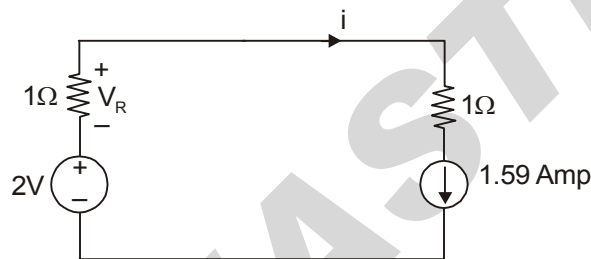
For  $t = 0^+$ ,  $S \rightarrow 2$ ,  $L \rightarrow$  current source



$$V_R = -i$$

$$V_R(0^+) = -i(0^+) = -1.59 \text{ Volts}$$

For  $t > 0$ ,  $S \rightarrow 2$

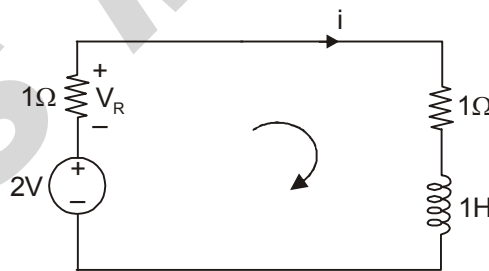

$$-2 + i + i + \frac{di}{dt} = 0$$

$$\frac{di}{dt} = 2[1 - i(t)]$$

At  $t = 0^+$

$$\frac{di}{dt}(0^+) = 2[1 - i(0^+)] = -1.18 \text{ A / sec}$$

As  $V_R = -i$

$$\frac{d}{dt} V_R(0^+) = -\frac{d}{dt} i(0^+) = 1.18 \text{ V / sec}$$

23. (c)

$$X_C = \frac{1}{2\pi fC}$$

When  $X_C = 0$ ,  $Z_1 = R_1$

$$I_1 = \frac{V}{R_1} \quad \theta_1 = \tan^{-1}\left(\frac{1}{\omega CR}\right) = \tan^{-1}\left(\frac{-X_C}{R}\right) = 0$$

$$\bar{I} = \bar{I}_1 + \bar{I}_2$$

as,  $C \downarrow X_C \uparrow$

$$Z_1 = \sqrt{R^2 + X_C^2} \uparrow \Rightarrow I_1 \downarrow \text{ and}$$

$$\theta_1 = \tan^{-1}\left(-\frac{X_C}{R}\right) \uparrow_{se}$$

&  $I_2 = \text{constant}$

$$I = I_1 + I_2$$

as  $I_1 \downarrow \quad I \downarrow$

at  $X_C = \infty \Rightarrow C = 0$

$$I_1 = 0 \quad I = I_2$$

$$\theta_1 = -90^\circ$$

24. (b)

Since the current  $V_x/4000A$  passes through  $2k\Omega$  and  $4V$  source and no current in  $3k\Omega$  resistor.

The KVL equation

$$4 + (2 \times 10^3) \left( \frac{V_x}{4000} \right) + 3 \times 10^3 \times (0) - V_x = 0$$


or  $4 + \frac{V_x}{2} - V_x = 0 \quad \therefore V_x = 8V$

or  $V_x = V_{Th}$

**To find  $R_{Th}$**

Due to the presence of dependent source  $R_{Th}$  cannot be obtained directly. So it is obtained by finding short circuit current  $I_{SC}$ , then

$$R_{Th} = \frac{V_{OC}}{I_{SC}}$$

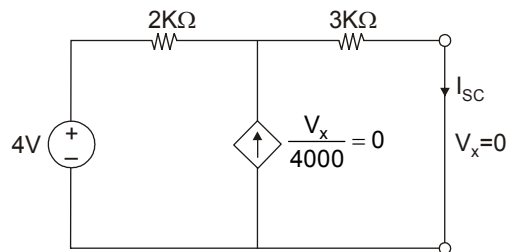


Here,  $I_{SC} = \frac{4}{(2+3)K} = 0.8 \times 10^{-3} A$

Therefore,  $R_{Th} = \frac{V_{OC}}{I_{SC}} = \frac{8}{0.8 \times 10^{-3}} = 10K\Omega$

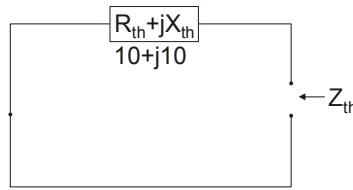25. (c)

For  $Z_{th}$  (equivalent thevenin impedance across load).



$$Z_{th} = 10 + j10 \quad \dots(i)$$

for maximum power consumed in the load, when  $X_L$  is variable

$$\frac{dP_L}{dX_C} = 0$$

$$\therefore X_C = -X_{th}$$

$$\therefore X_C = -j10\Omega$$

therefore load impedance  $Z_L = 10 - j10$  from equation (i)

so maximum load power  $P_{max} = (I_{max})^2 R_L \quad \dots(ii)$

when  $R_L = 10\Omega$  &  $X_C = 10\Omega$

then  $I = I_{max}$

$$I = \frac{V_{th}}{10 + j10 + 10 - jX_C}$$

$$I = I_{max} = \frac{100 \angle 0^\circ}{10 + j10 + 10 - j10}$$

$$= \frac{100}{20} = 5A$$

so, from equation (ii)

$$P_{max} = (5)^2 \times 10$$

$$P_{max} = 250 \text{ W}$$

**Note :** We can use,


$$P_{max} = \frac{V_{th}^2}{4R_L} \text{ here, it is also valid.}$$

but it is not recommended to use  $\frac{V_{th}^2}{4R_L}$  when impedance is given.

26. (a)


By super position theorem

Using 3A current source only :

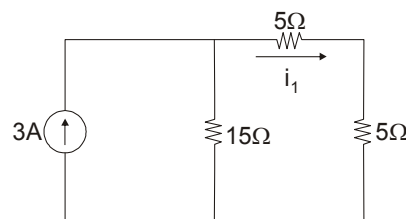

$$i_1 = 3 \times \left( \frac{15}{15 + 10} \right) = 1.8A$$

Using 5A current source only :

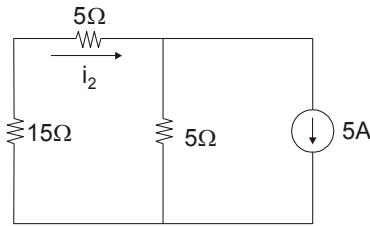

⇒

$$i_2 = \left( \frac{5}{20+5} \right) \times 5 = 1A$$


Therefore,

$$\frac{i_2}{i_x} \times 100 = \frac{1}{(1.8+1)} \times 100 = 35.714\%$$

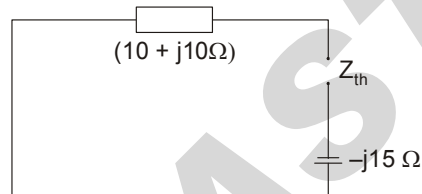27. (a)

Since  $R_L$  is variable

$Z_{th}$  across  $R_L$  is by short circuiting  $100\angle 0^\circ$  V source, we get



$$Z_{th} = 10 + j10 - j15$$


$$Z_{th} = 10 - j5$$

so,

$$R_L = |Z_{th}| = \sqrt{10^2 + 5^2} = 5\sqrt{5} \Omega$$


For  $V_{th}$

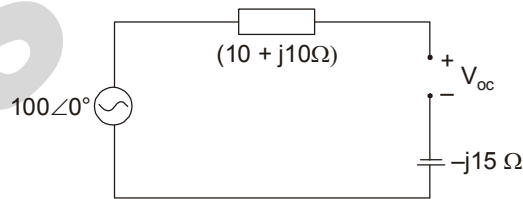open circuit voltage across terminal of  $R_L$  is



$$V_{oc} = 100\angle 0^\circ \quad (\text{as no current flow in the circuit})$$

so, Thevenin equivalent circuit is

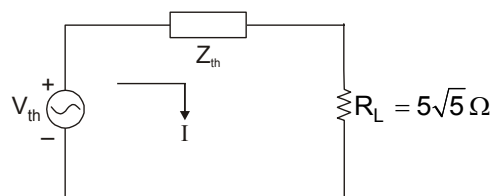

if,  $R_L = 5\sqrt{5} \Omega$  then  $I = I_{max}$  and corresponding power consumed in  $R_L$  will be maximum

so,

$$\begin{aligned} P_{max} &= I_{max}^2 R_L \\ &= \frac{(100\angle 0^\circ)^2}{(Z_{th} + R_L)^2} \times R_L \end{aligned}$$




$$\begin{aligned} \therefore I &= I_{\max} = \frac{V_{th}}{Z_{th} + R} \\ &= \frac{(100)^2}{(10 - j5 + 5\sqrt{5})^2} \times (5\sqrt{5}) \\ &= \frac{(100)^2}{|21.18 - j5|^2} \times (5\sqrt{5}) \\ &= \frac{(100)^2}{(21.76)^2} \times 5\sqrt{5} \\ P_{\max} &= 236 \text{ W} \end{aligned}$$

**Note :** If impedance is given don't use

$$P_{\max} = \frac{V_{th}^2}{4R_L}$$

28. (b)

To find  $R_{Th}$

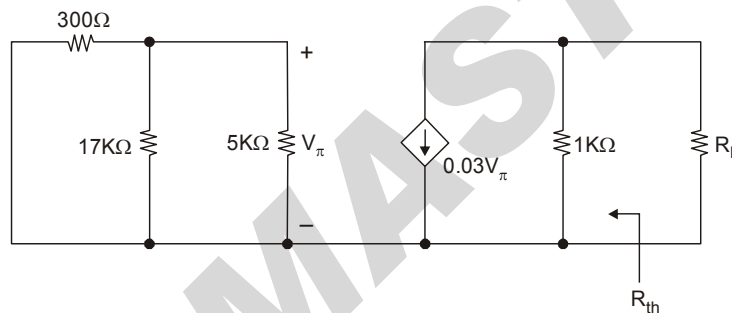


Here,  $V_{\pi} = 0 \Rightarrow 0.03V_{\pi} = 0$

$$\therefore R_{Th} = 1K\Omega$$

Thus for maximum power transfer to  $R_L$ ,

$$R_L = R_{Th} = 1K\Omega$$

To find  $V_{Th} = V_{OC}$

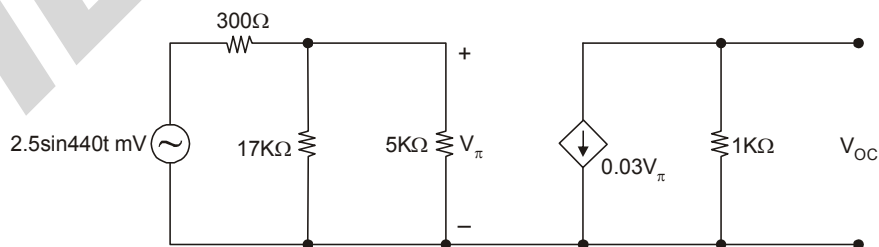

$$V_{OC} = -0.03V_{\pi}(1000) = -30V_{\pi}$$

where 
$$V_{\pi} = (2.5 \times 10^{-3} \sin 440t) \times \left( \frac{3864}{3864 + 300} \right)$$


**Note :**  $17K\Omega \parallel 5K\Omega = 3.864K\Omega$

Now, 
$$V_{OC} = V_{Th} = -30V_{\pi} = -30 \times 2.5 \times 10^{-3} \times \frac{3864}{(3864 + 300)} \sin 440t$$

$$= -69.596 \sin 440t \text{ mV}$$

$$P_{\max} = \frac{V_{\text{Th}}^2}{4R_{\text{Th}}} = \frac{1.211 \sin^2 440t \mu\text{W}}{1} = 1.211 \mu\text{W}$$

29. (c)

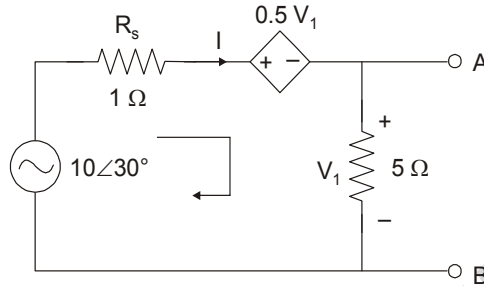

let the current in the circuit is I

$$V_1 = 5I \Rightarrow V_{\text{OC}} = V_1 = 5I \quad \dots(\text{i})$$

using KVL in loop, we get,

$$10\angle 30^\circ - I \times 1 - 0.5(5I) - 5I = 0$$


$$\Rightarrow I = \frac{10\angle 30^\circ}{8.5} \quad \dots(\text{ii})$$

from equation (i) and equation (ii)

$$V_{\text{OC}} = 5I = \frac{10\angle 30^\circ}{1.7} \text{ volt} \quad \dots(\text{iii})$$

for  $I_{\text{sc}}$

Short cricuiting the terminal AB,

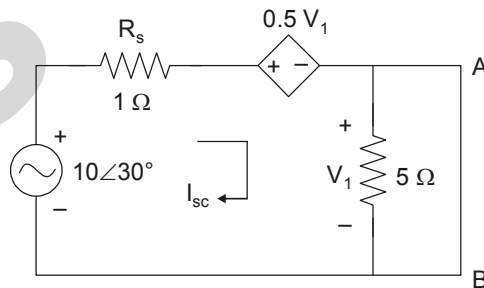

due to short circuit,

$$V_1 = 0 \quad \dots(\text{iv})$$

using KVL in the loop

$$10\angle 30^\circ = I_{\text{sc}} R_s \quad \dots(\text{v})$$

$$\Rightarrow I_{\text{sc}} = \frac{10\angle 30^\circ}{1} = 10\angle 30^\circ \quad \dots(\text{vi})$$

$$\therefore Z_{\text{th}} = \frac{V_{\text{OC}}}{I_{\text{sc}}} = \frac{10\angle 30^\circ}{10\angle 30^\circ} = 0.588 \Omega$$


if  $R_s = 0 \Omega$  then  $Z_{\text{th}} = 0$  because from equation (v)

$$I_{sc} = \frac{10 \angle 30^\circ}{R_s} = \frac{10 \angle 30^\circ}{0} = \infty$$

$$\Rightarrow Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{V_{oc}}{\infty} = 0 \Omega$$

30. (c)

By connecting 1A current source at input

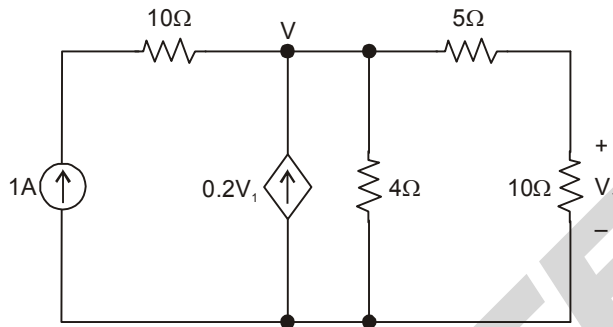

By KCL

$$\frac{V}{4} + \frac{V}{15} = 1 + 0.2V_1$$

or

$$\frac{V}{4} + \frac{V}{15} = 1 + 0.2 \left( \frac{V}{15} \right) \times 10$$

or

$$\frac{V}{4} + \frac{V}{15} - \frac{2V}{15} = 1$$

or

$$\frac{11}{60} V = 1 \Rightarrow V = \frac{60}{11}$$


Voltage across 1A current source

$$V_{in} = V + 1 \times 10 = \frac{60}{11} + 10 = \frac{170}{11}$$

∴

$$Z_{in} = \frac{V_{in}}{1} = \frac{170}{11} \Omega$$

31. (d)

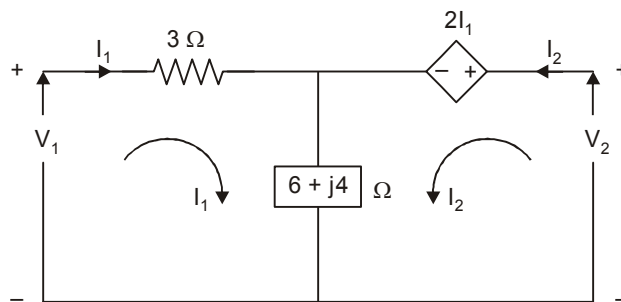

KVL eq. in loop (i)

$$V_1 = 3I_1 + (6 + j4)I_1 + (6 + j4)I_2$$

$$V_1 = (9 + j4)I_1 + (6 + j4)I_2$$

...(i)

KVL equation in loop (ii),

$$-V_2 + 2I_1 + (6 + j4)I_2 + (6 + j4)I_1 = 0$$

$$\Rightarrow V_2 = (8 + j4)I_1 + (6 + j4)I_2 \quad \dots(ii)$$

since,

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \dots(iii)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \dots(iv)$$

comparing (i) with (iii) and eq. (ii) with eq. (iv) we get,

$$[z] = \begin{bmatrix} 9 + j4 & 6 + j4 \\ 8 + j4 & 6 + j4 \end{bmatrix}$$

32. (b)

By definition of y-parameters :

$$I_1 = 0.1V_1 - 0.0025V_2 \quad \dots(1)$$

$$I_2 = -8V_1 + 0.05V_2 \quad \dots(2)$$

$$\frac{1 - V_1}{2} = I_1 \quad \dots(3)$$

and

$$I_2 = \frac{-V_2}{5} \quad \dots(4)$$

From eqn. (4) and (2)

$$\frac{-V_2}{5} = -8V_1 + 0.05V_2$$

∴

$$8V_1 = 0.05V_2 + \frac{V_2}{5}$$

or

$$8V_1 = 0.25V_2$$

∴

$$\frac{V_2}{V_1} = \frac{8}{0.25}$$

or

$$\boxed{\frac{V_2}{V_1} = 32}$$

33. (d)

- Since  $I_1$  and  $I_2$  are not independent in circuit (I) the Z parameter can not be found.
- Y parameter of circuit I:

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

with

$$V_2 = 0, \quad I_1 = -I_2 \quad \text{and} \quad V_1 = I_1 R$$

$$\left. \frac{I_1}{V_1} \right|_{V_2=0} = Y_{11} = \frac{1}{R} \quad \text{and} \quad \left. \frac{I_2}{V_1} \right|_{V_2=0} = -\frac{1}{R} = Y_{21}$$

For circuit II,

- Since  $V_1$  and  $V_2$  are not independent, the Y parameters can not be found.
- For Z parameter (Circuit II):

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Put

$$I_2 = 0$$

$$V_1 = V_2 \quad \text{and} \quad V_1 = I_1 R \quad \dots(i)$$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = R = Z_{11} \quad \text{from eq. (i)}$$


$$\left. \frac{V_2}{I_1} \right|_{I_2=0} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_{11} = Z_{21} = R$$

34. (a)

By definition,

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

To obtain  $y_{21}$

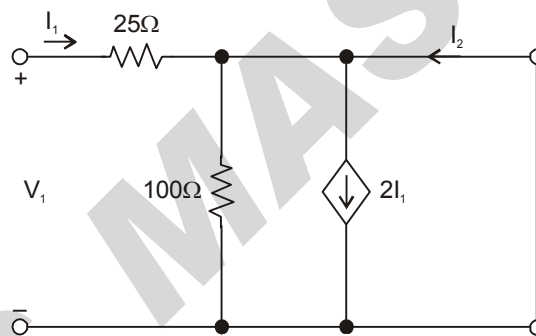

By KCL

$$I_1 + I_2 = 2I_1$$

or

$$I_2 = I_1$$

$$\frac{I_2}{V_1} = \frac{I_1}{V_1} = \frac{1}{25} = 0.045$$

Alternatively :

$$I_1 = \frac{V_1 - V_2}{25} = 0.04V_1 - 0.04V_2 \quad \dots(1)$$

and

$$I_1 + I_2 = \frac{V_2}{100} + 2I_1$$

or

$$I_2 = \frac{V_2}{100} + I_1 = 0.01V_2 + 0.04V_1 - 0.04V_2$$


or

$$I_2 = 0.04V_1 - 0.03V_2$$

∴

$$y_{21} = 0.04$$

35. (d)

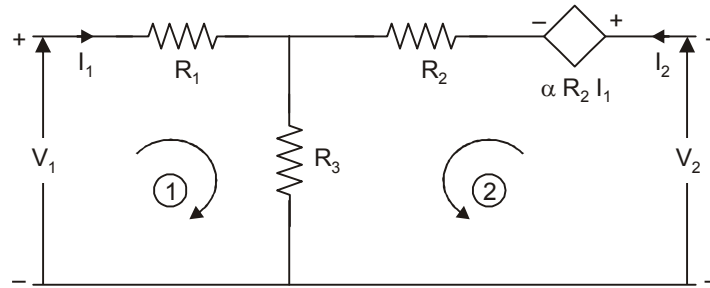

by KVL in loop (i),

$$V_1 = (R_1 + R_3)I_1 + R_3I_2 \quad \dots(i)$$

by KVL in loop (ii),

$$V_2 = (\alpha R_2 + R_3)I_1 + (R_2 + R_3)I_2 \quad \dots(ii)$$

On comparing equation (i) and (ii) with standard equation of Z parameter, we have

$$Z_{11} = R_1 + R_3 \quad \dots(iii)$$

$$Z_{12} = R_3 \quad \dots(iv)$$


$$Z_{21} = \alpha R_2 + R_3 \quad \dots(v)$$

$$Z_{22} = R_2 + R_3$$

as,

- $Z_{12} \neq Z_{21} \Rightarrow$  Network is not reciprocal
- $Z_{11} \neq Z_{22} \Rightarrow$  Network is not symmetrical
- $Z_{21} = \alpha R_2 + Z_{12}$  (option c is wrong) – from eq. (iv) and (v)
- $Z_{11} - Z_{12} = R_1$  (option d is true) – from eq. (iii) and (iv)

36. (b)

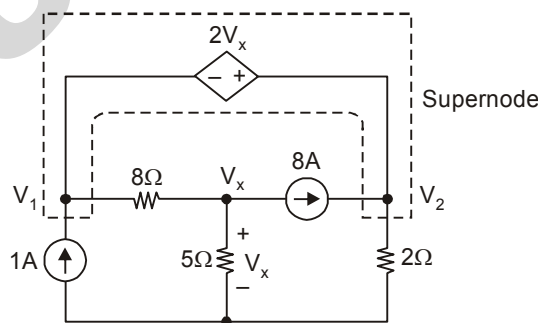

By KCL

$$\frac{V_1 - V_x}{8} + \frac{V_2}{2} = 1 + 8$$

or,  $V_1 - V_x + 4V_2 = 72 \quad \dots(1)$

and  $\frac{V_x - V_1}{8} + \frac{V_x}{5} = -8$

or  $-5V_1 + 13V_x = -320 \quad \dots(2)$

and from super node

$$V_2 - V_1 = 2V_x$$

$$\text{or, } V_1 - V_2 + 2V_x = 0 \quad \dots(3)$$

From eqn. (2),

$$V_1 = \frac{13V_x + 320}{5}$$

Substituting in eqn. (1) and (3)

$$\frac{13V_x + 320}{5} - V_x + 4V_2 = 72$$

$$\text{or } 8V_x + 20V_2 = 40 \quad \dots(4)$$

$$\text{and } \frac{13V_x + 320}{5} - V_2 + 2V_x = 0$$

$$\text{or } 23V_x - 5V_2 = -320 \quad \dots(5)$$

$$\text{Eq. (4) } 8V_x + 20V_2 = 40$$

$$+ \text{Eq. (5)} \times 4 \quad 92V_x - 20V_2 = -1280$$

$$100V_x = -1240$$

$$\text{or } V_x = -12.4 \text{ V}$$

$$\therefore V_1 = \frac{13V_x + 320}{5} = \frac{13 \times (-12.4) + 320}{5}$$


$$\text{or } V_1 = 31.76 \text{ V}$$

Therefore power supplied by 1A source

$$P = (V_1) \times 1 = 31.76 \text{ W}$$

37. (a)



By  $\gamma - \Delta$  conversion

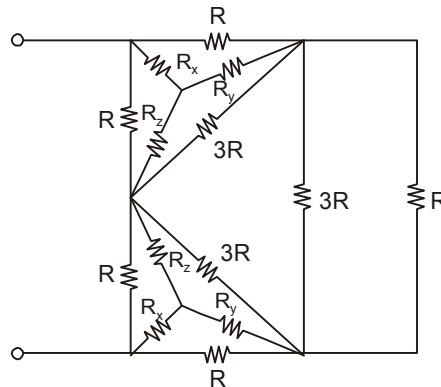

$$R_x = \frac{R \times R}{R + R + 3R} = \frac{R}{5}$$


$$R_y = R_z = \frac{R \times 3R}{R + R + 3R} = \frac{3R}{5}$$

Thus,

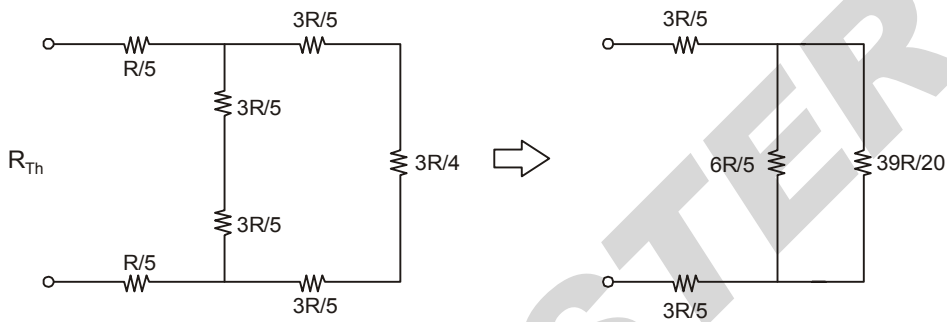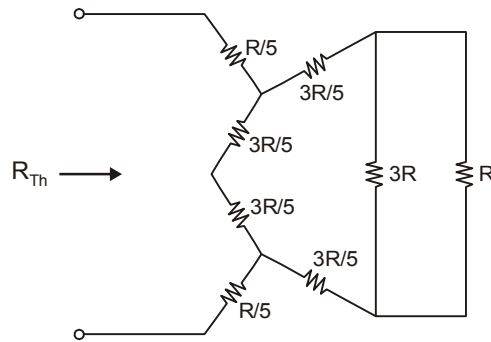

$$\frac{6R}{5} \parallel \frac{39}{20}R = \frac{\frac{6R}{5} \times \frac{39}{20}R}{\frac{6R}{5} + \frac{39}{20}R} = \frac{26}{35}R$$

The circuit reduces as

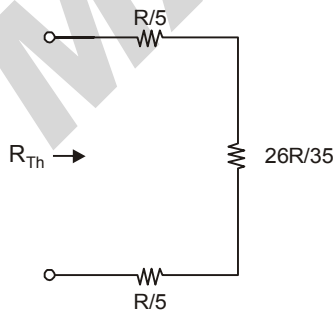


$$R_{Th} = \frac{R}{5} + \frac{26}{35}R + \frac{R}{5}$$

$$R_{Th} = \frac{40}{35}R = 1.1428R$$


or  $R_{Th} = 1.143\Omega$

38. (c)


By source transformation

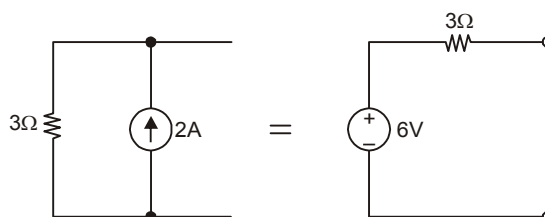



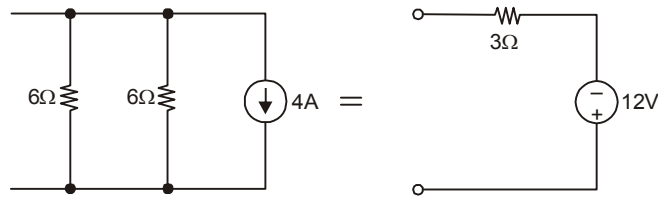


Thus,

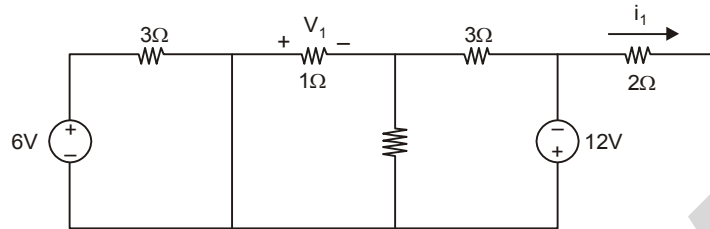

$$V_1 = \left( \frac{1}{1+3+3} \right) \times 18 = \frac{18}{7} = 2.571V$$

Now, in the original circuit

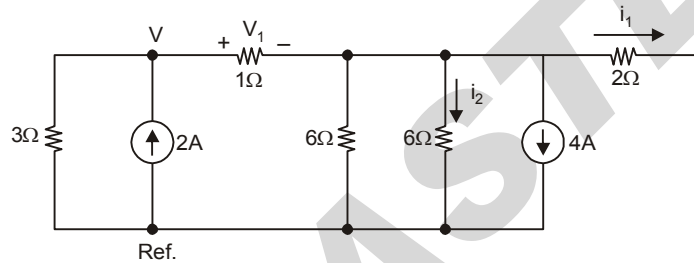

By nodal analysis

$$\frac{V}{3} - 2 + \frac{V_1}{1} = 0$$

$$\text{or } \frac{V}{3} - 2 + 2.571 = 0$$

$$\text{or } V = -1.7143 \text{ Volts}$$

$$\text{Voltage across } 6\Omega \text{ resistor} = V - V_1 = -4.2853 \text{ Volts}$$

$$\therefore i_2 = \frac{-4.2853}{6} = -0.7142 \text{ A}$$


Alternatively:

$$i_2 = \left( \frac{18}{7} - 4 \right) \times \frac{1}{2} = -0.7142 \text{ A}$$

Since,  $i_1 = 0$

$$\therefore i_1 + i_2 = -0.7142 \text{ A}$$

39. (a)

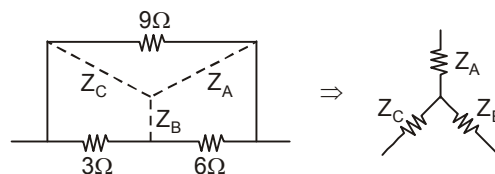

Using conversion delta star


$$Z_A = \frac{9 \times 6}{9+6+3} \quad Z_C = \frac{9 \times 3}{9+6+3} \quad Z_B = \frac{6 \times 3}{9+6+3}$$

$$Z_A = 3\Omega$$

$$Z_C = 1.5\Omega$$

$$Z_B = 1$$

The given circuit become as

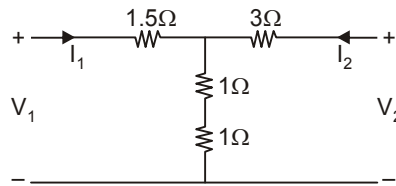

Using KVL equation at input loop

$$V_1 = (1.5+2)I_1 + 2I_2 \quad \dots(1)$$

Using KVL equation at output loop

$$V_2 = (3+1+1) I_2 + 2I_1 \quad \dots(2)$$

Since,

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \dots(3)$$

$$\& \quad V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \dots(4)$$

On comparing equation (1) with (3) and equation (2) with (4)


$$Z_{11} = 3.5\Omega$$

$$Z_{12} = 2\Omega$$

$$Z_{21} = 5\Omega$$

$$Z_{22} = 2\Omega$$

40. (a)

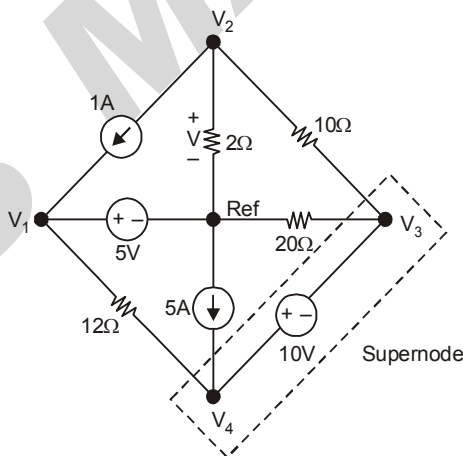

By inspection,  $V_1 = 5 \text{ V} \quad \dots(1)$

Nodes 3 and 4 from a super node. Thus by KCL

$$\frac{V_2}{2} + \frac{V_2 - V_3}{10} = -1$$

$$\text{or } 6V_2 - V_3 = -10 \quad \dots(2)$$

$$\frac{V_3 - V_2}{10} + \frac{V_3}{20} + \frac{V_4 - V_1}{12} = 5$$

$$\text{or } -5V_1 - 6V_2 + 9V_3 + 5V_4 = 300$$

$$\text{or } -6V_2 + 9V_3 + 5V_4 = 325 \quad \dots(3)$$

Also at supernode,

$$V_4 - V_3 = 10 \quad \dots(4)$$

$$\text{From eqn. (2), } V_3 = 6V_2 + 10 \quad \dots(5)$$

$$\begin{aligned} \text{From eqn. (4), } V_4 &= 10 + V_3 \\ &= 10 + 6V_2 + 10 \\ &= 6V_2 + 20 \quad \dots(6) \end{aligned}$$

Substituting  $V_3$  and  $V_4$  in Eqn. (3)

$$-6V_2 + 9(6V_2 + 10) + 5(6V_2 + 20) = 325$$

$$\text{or } 78V_2 = 135$$

$$\text{or } V_2 = 1.73077V$$

$$\text{Since, } V_2 = V$$

$$\text{So, } V = 1.731 V \text{ [upto three decimal places]}$$

41. (b)

Thevenin equivalent circuit across  $10\Omega$  in series with  $100V$  battery are drawn in figure 1 and figure (2)

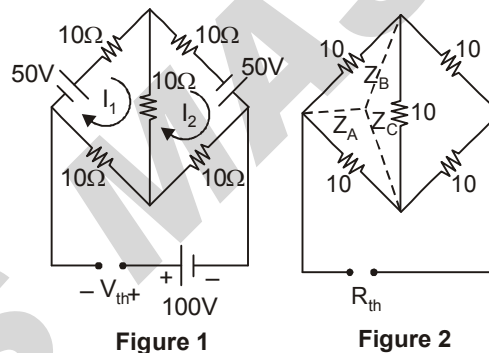


Figure 1

Figure 2

In figure (1) by applying KVL equation in loop (1) and loop (2)

We get

$$50 = 30 I_1 - 10 I_2 \quad \dots(1)$$

and

$$50 = -10 I_1 + 30 I_2 \quad \dots(2)$$

On solving equation (1) and (2)

$$I_1 = I_2 = 2.5A$$

For the mesh containing  $V_{th}$  we have

$$100 - V_{th} + 10(I_1) + 10(I_2) = 0$$

or


$$V_{th} = 100 + 10(2.5) + 10(2.5)$$

$$V_{th} = 150 V$$

From figure (2) we get

Using  $\Delta - Y$  conversion
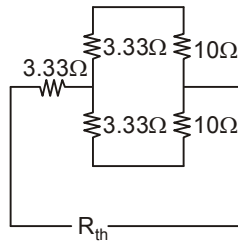
$$Z_A = Z_B = Z_C = \frac{10 \times 10}{10 + 10 + 10} = \frac{10}{3} \Omega$$




$$R_{th} = 3.33 + (10 + 3.33) \parallel (10 + 3.33) \Omega = 10 \Omega$$

Alternatively:

$$R_{th} = 10 \Omega \text{ as bridge is balanced}$$


So

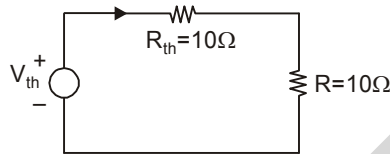

$$I = \frac{V_{th}}{R_{th} + R} = \frac{150}{10 + 10} = 7.5 \text{ A}$$

42. (a)

Given circuit is

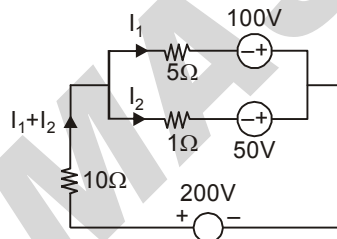

Applying KVL to the loops, for the assumed directions of current flow we obtain.

$$5I_1 - 100 + 50 - I_2 = 0$$

$$\& \quad -200 + 10(I_1 + I_2) + 5I_1 - 100 = 0$$

$$\text{Thus, } 5I_1 - I_2 = 50 \quad \text{and} \quad 15I_1 + 10I_2 = 300$$

on solving

$$I_1 = 12.3077 \text{ A, } I_2 = 11.538 \text{ A}$$


$$P_{50V} = I_2 \times 50 = 11.538 \times 50 = 576.9 \text{ W (supplied)}$$

$$P_{100V} = I_1 \times 100 = 1230.77 \times 100 = 1230.77 \text{ W (supplied)}$$

$$P_{200V} = (I_1 + I_2) \times 200 = 23.8457 \times 200 = 4769.14 \text{ W (supplied)}$$

43. (c)

Using mesh analysis

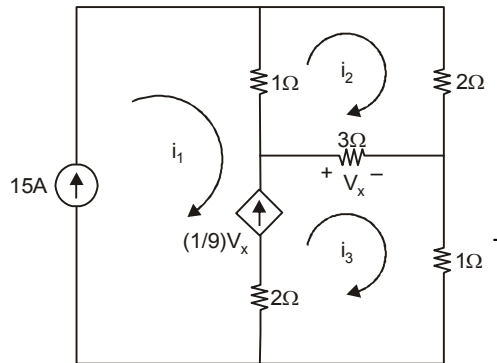

In mesh 3; ....(1)

$$\frac{V_x}{9} = i_3 - i_1$$

As  $V_x = (i_3 - i_2)3$

$$\therefore -i_1 + \frac{i_2}{3} + \frac{2i_3}{3} = 0$$

or  $i_2 + 2i_3 = 45$  (using  $i_1 = 15A$ ) ....(2)

In mesh 2

$$(i_2 - i_1) \times 1 + 2i_2 + 3(i_2 - i_3) = 0$$

or  $6i_2 - 3i_3 = 15$

or  $2i_2 - i_3 = 5$  .....(3)


Solving (2) and (3), we get

$$i_2 = 11A, \quad i_3 = 17A$$

Now,  $V_x = 3(i_3 - i_2) = 3(17 - 11) = 18V$

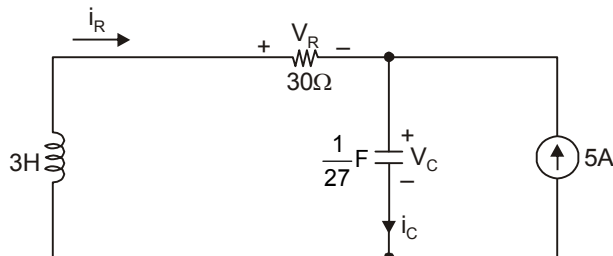44. (b)

For  $t < 0$ ,  $4u(t) = 0$ , therefore the circuit reduces to



circuit is assumed to be in steady state so

$$V_L(0^-) = 0 \text{ [short circuit]}$$

$$I_C(0^-) = 0 \text{ [open circuit]}$$

$$i_R(0^-) = -5A$$

$$V_R(0^-) = -5 \times 100 = -150V$$


$$V_C(0^-) = 150V$$

$$i_L(0^-) = -i_R(0^-) = 5A$$

At  $t = 0^+$ :

Current in inductor and voltage in capacitor do not change instantaneously, so  $i_L(0^+) = 5A$ ,  $V_C(0^+) = 150V$ .

The circuit can be represented as

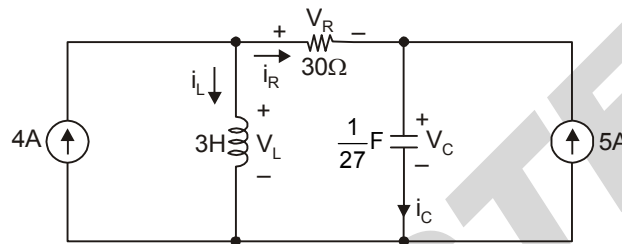

At left node, by KCL

$$4 = i_L + i_R = 5 + i_R$$

$$\therefore i_R = -1A$$

$$\therefore V_R(0^+) = (-1) \times 30 = -30V$$

$$i_C(0^+) = -1 + 5 = 4A$$

$$\begin{aligned} V_L(0^+) &= V_R(0^+) + V_C(0^+) \\ &= -30 + 150 = 120V \end{aligned}$$


Thus,  $V_L(0^+) = 120V$ ,  $V_R(0^+) = -30V$ ,  $i_C(0^+) = 4A$

45. (c)

To find impulse response,

$$V_{in} = \delta(t)$$

$$\therefore H(s) = \frac{V_0(s)}{1}$$

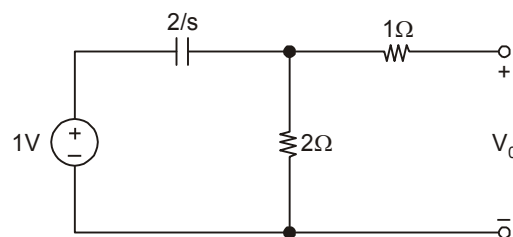

To find  $H(s)$

Therefore,  $V_0|_{V_{in}=\delta(t)} = \frac{2}{\frac{2}{s} + 2} = \frac{s}{s+1} = H(s)$

Now, if  $V_{in} = 6e^{-t}u(t)$

$\therefore V_0(t) = L^{-1}\{V_{in}(s)H(s)\}$

Since,  $V_{in}(s) = \frac{6}{s+1}$


$\therefore V_0 = \left(\frac{6}{s+1}\right)\left(\frac{s}{s+1}\right) = \frac{6s}{(s+1)^2}$

By partial fraction expansion,

$$V_0 = \frac{A}{s+1} + \frac{B}{(s+1)^2} = \frac{6}{s+1} - \frac{6}{(s+1)^2}$$

$\therefore V_0(t) = (6e^{-t} - 6te^{-t})u(t)$   
 $= 6e^{-t}(1-t)u(t)$

46. (d)

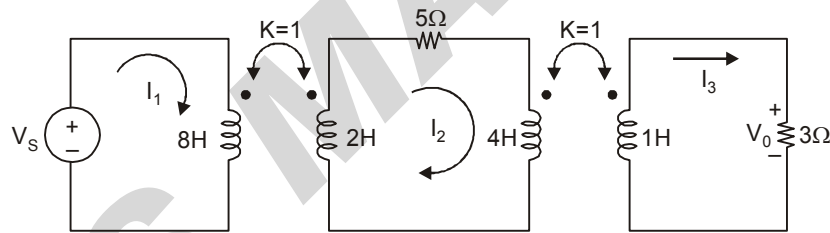

Mutual inductance  $= K\sqrt{L_1L_2}$

Between  $L_1 = 8H$  and  $L_2 = 2H$ ,  $M_{12} = \sqrt{8 \times 2} = 4H$

Between  $L_3 = 4H$  and  $L_4 = 1H$ ,  $M_{34} = \sqrt{4 \times 1} = 2H$

By KVL

$V_s = j8\omega I_1 - j4\omega I_2 \dots(1)$

$0 = -j4\omega I_1 + (5 + j\omega 6)I_2 - j2\omega I_3 \dots(2)$

$0 = -j2\omega I_2 + (3 + j\omega)I_3 \dots(3)$

$V_0 = 3I_3 \Rightarrow$  It is better to obtain  $I_3$ .

From eq. (3)

$$I_2 = \frac{3 + j\omega}{2j\omega} I_3$$

From eqn. (1)

$$I_1 = \left[ V_s + j4\omega \left( \frac{3+j\omega}{2j\omega} \right) I_3 \right] \frac{1}{j8\omega}$$

$$I_1 = \frac{1}{j8\omega} [V_s + (6+2j\omega)I_3]$$

Substituting in eq. (2)

$$0 = \frac{-j4\omega}{j8\omega} [V_s + (6+2j\omega)I_3] + (5+j2\omega) \times \frac{(3+j\omega)}{j2\omega} I_3 - j2\omega I_3$$

or 
$$I_3 \left[ -\frac{(6+j2\omega)}{2} + \frac{(15-6\omega^2+j23\omega)}{j2\omega} - j2\omega \right] = \frac{V_s}{2}$$


or 
$$I_3 \left[ \frac{-j6\omega + 2\omega^2 + 15 - 6\omega^2 + j23\omega - 4\omega^2}{j2\omega} \right] = \frac{V_s}{2}$$

$$I_3 \left[ \frac{15 + j17\omega}{j\omega} \right] = V_s$$

Since,  $V_0 = 3I_3$

$\therefore \frac{V_0}{V_s} = \frac{j3\omega}{15 + j17\omega}$

47. (a)  
At  $t > 0$

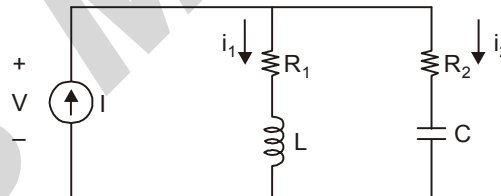

$$I = i_1 + i_2 \quad \dots(1)$$

$$V = R_1 i_1 + L \frac{di_1}{dt} \quad \dots(2)$$

$$V = i_2 R_2 + \frac{1}{C} \int i_2 dt \quad \dots(3)$$

Differentiating equation (3) wrt time

$$\frac{dv}{dt} = \left( \frac{di_2}{dt} \right) R_2 + \frac{1}{C} i_2 \quad \dots(4)$$

Equation (3) can also be written as

$$V = i_2 R_2 + V_C$$


$$\frac{dv}{dt} = \left( \frac{di_2}{dt} \right) R_2 + \frac{dV_C}{dt} \quad \dots(5)$$

From equation (4) and (5)

$$\frac{dV_C}{dt} = \frac{i_2}{C} \Rightarrow \frac{dV_C(0^+)}{dt} = \frac{I_2(0^+)}{C} \quad \dots(6)$$



At  $t = 0^+$

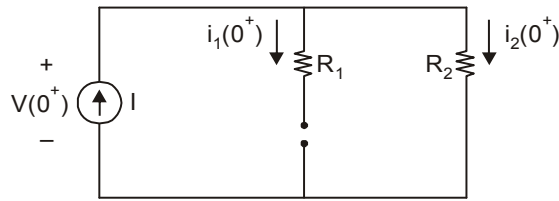

$$V(0^+) = i_2(0^+) \cdot R_2$$

$$I = i_1(0^+) + i_2(0^+)$$

$$i_1(0^+) = 0$$

$$\dots(7) \Rightarrow i_2(0^+) = I$$

$$V(0^+) = I \cdot R_2$$

from (2) and (7)

$$\left. \frac{di_1}{dt} \right|_{t=0^+} = \frac{+R_2 I}{L} = \frac{5 \times 5}{.1} = 250 \text{ A/sec.}$$

from equation (6)

$$\begin{aligned} \left. \frac{dv_c}{dt} \right|_{t=0^+} &= \frac{i_2(0^+)}{C} = \frac{I}{C} \\ &= \frac{5}{2.5\text{m}} = 2000 \text{ V/sec.} \end{aligned}$$


48. (d)

For  $t < 0$

$$V = \left( \frac{100}{100 + 50} \right) \times 3 = 2 \text{ Volts}$$

$$\text{Current in inductor} = \frac{5}{500} = 10 \text{ mA}$$

At  $t = 0^+$ , the circuit becomes

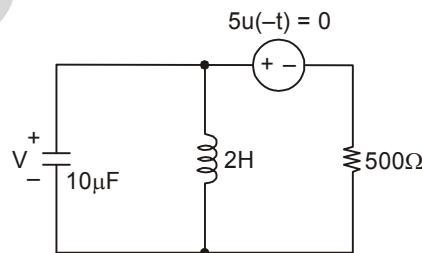

Now, by nodal analysis

$$\frac{1}{L} \int V dt + C \frac{dV}{dt} + \frac{V}{500} = 0$$

As current in inductor can't change instantaneously; so at  $t = 0^+$

$$\frac{1}{L} \int V dt = 10 \text{ mA}$$

Therefore,



$$10 \times 10^{-3} + C \frac{dV}{dt} + \frac{V}{500} = 0$$

$$\text{or } \frac{dV}{dt} = -\frac{2}{10 \times 10^{-6} \times 500} - \frac{10 \times 10^{-3}}{10 \times 10^{-6}} = -1400 \text{ V/s}$$

49. (c)

**Case I** $t < 0$ 

Switch at position 1, circuit under steady state (capacitor O.C.)

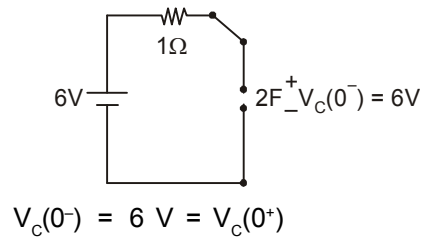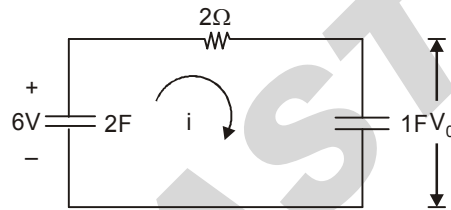**Case II** $t > 0$ 

Using KVL equation

$$\frac{1}{2} \int i \, dt + \int i \, dt + 2i = 6$$

Taking Laplace transfer

$$\frac{1}{2} \frac{I(s)}{s} + 2I(s) + \frac{I(s)}{s} = \frac{6}{s}$$

$$I(s) = \frac{6}{2s + 1.5}$$

$$I(s) = \frac{6/2}{s + 0.75} = \frac{3}{s + 0.75}$$

Taking inverse Laplace

$$i(t) = 3e^{-0.75t}$$

$$V_0(t) = \int_0^t i \, dt$$

$$= \int_0^t 3e^{-0.75t} \, dt$$

$$= 3 \int_0^t e^{-0.75t} \, dt = \frac{3}{0.75} [1 - e^{-0.75t}]$$

$$V_0(t) = 4[1 - e^{-0.75t}]$$


$$V_0(t) \Big|_{t=4/3 \text{ sec.}} = 4[1 - e^{-1}] = 2.528 \text{ V}$$

50. (d)

Case I

for  $t < 0$

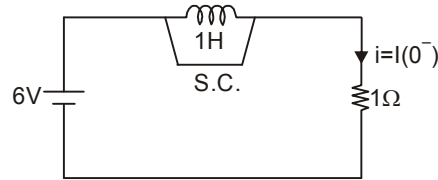Switch is at position 1 and inductor is S.C. and under steady state condition.



$$I(0^-) = 6/1 = 6A$$


⇒

$$I(0^-) = I(0^+) = 6A$$

Case II

$t > 0$

$$6A = I(0^+)$$

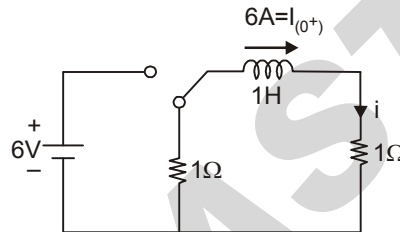

Current will decay exponentially

$$i(t) = I_0(0^+)e^{-t/\tau}$$

$$i(t) = 6e^{-t/\tau}$$

∴

$$\tau = \frac{L}{R} = \frac{1}{1+1} = 0.5 = \frac{1}{2}$$

$$i(t) = 6e^{-2t}A$$


At  $t = 0.1$  sec.

$$i(0.1) = 6 \times e^{-2 \times 0.1} = 4.912 A$$

$$w_L = \text{energy stored} = \frac{1}{2}L[i(0.1)]^2$$

$$= \frac{1}{2} \times 1 \times (4.912)^2 = 12.065 J$$

51. (a)

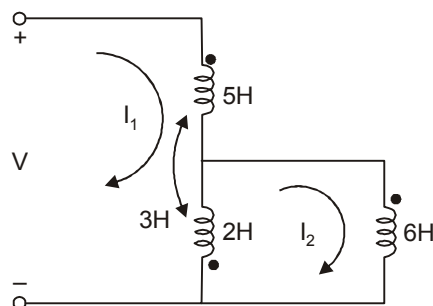

By KVL in Mesh-1 :

$$V = j5\omega l_1 - j3\omega(l_1 - l_2)$$

or  $V = j2\omega l_1 + j3\omega l_2 \quad \dots(1)$

In Mesh-2 :

$$j6\omega l_2 + j2\omega(l_2 - l_1) + j3\omega l_1 = 0$$

or  $j8\omega l_2 + j\omega l_1 = 0$

or  $I_2 = \frac{-l_1}{8} \quad \dots(2)$

Substituting in Eqn. (1), we get

$$V = j2\omega l_1 + j3\omega\left(\frac{-l_1}{8}\right) = \frac{j13\omega}{8}$$

$$\frac{V}{l_1} = Z_{in} = j\frac{13}{8}\omega$$

$$L_{eq} = \frac{13}{8} = 1.625$$


52. (d)  
 $t < 0$

$$V_c(0^-) = \frac{Q_0}{C} = \frac{2500\mu\text{C}}{50\mu\text{F}} = 50 \text{ V}$$


$\Rightarrow$

$$V_c(0^-) = V_c(0^+) = 50\text{V}$$

Draw circuit at  $t = (0^+)$

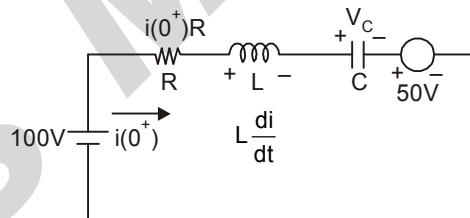

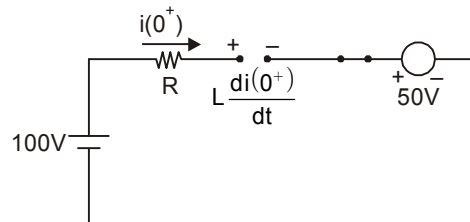Since at  $t = 0^+$  inductor behave as an open circuit and capacitor behave as short circuit.



as  $i(0^+) = 0$  circuit is open


So using KVL

$$-100 + L \left. \frac{di}{dt} \right|_{t=0^+} + 50 \Rightarrow 0$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = \frac{50}{L} = \frac{50}{0.1} = 500 \text{ A/sec.}$$

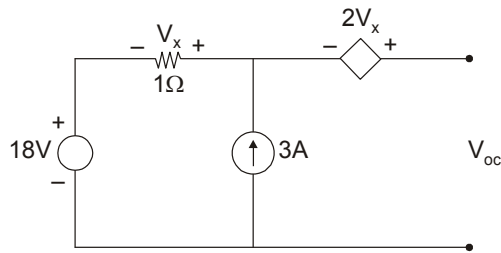53. (b)

$V_{th}$  is the open circuit voltage across terminal ab



Using KVL equation.


$$18 + V_x + 2V_x - V_{oc} = 0$$

$$\Rightarrow V_{oc} = 18 + 2V_x + V_x$$

$$\therefore V_x = +3 \times 1 \text{ V}$$

$$\Rightarrow V_{oc} = 18 + 3(+3) = 27\text{V}$$

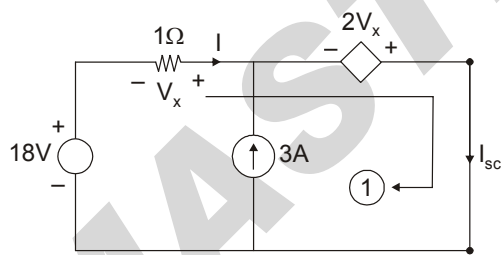By short circuiting the  $6\Omega$  resistor



Using KVL equation in given loop (1)

$$18 + V_x + 2V_x = 0$$

$$\Rightarrow V_x = -6\text{V}$$

The current through  $1\Omega$  resistor is I

$$I = \frac{6}{1} = 6\text{A}$$


So  $I_{sc} = I + 3 = 9\text{A}$

Thus


$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

$$R_{th} = \frac{27}{9} = 3\Omega$$


54. (a)

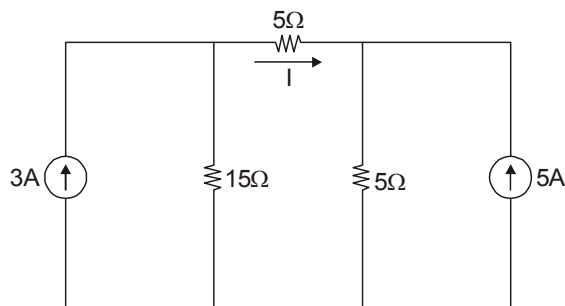

Using 3A source only :

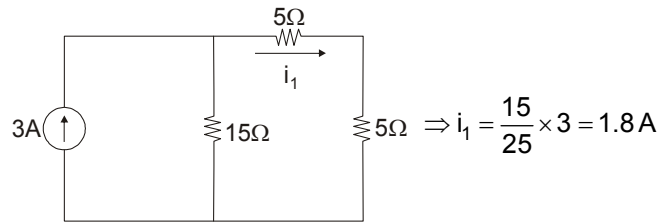

Using 5A source only :

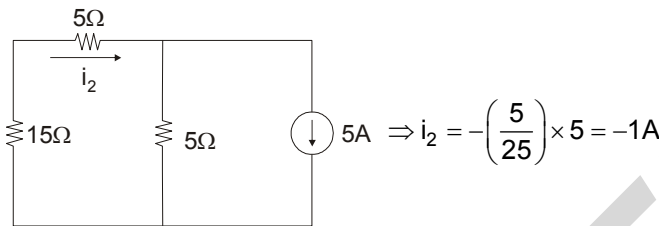


Therefore,  $i = i_1 + i_2 = 1.8 - 1 = 0.8A$

∴ Statement 1 is correct.

Superposition theorem doesn't apply to power as power is a nonlinear quantity. Hence statement 2 is not correct.

55. (a)

Given circuit

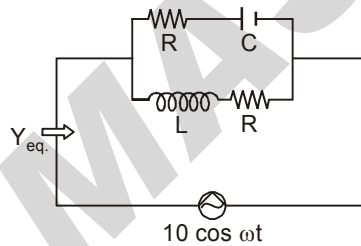

∴

$$Y_1 = \frac{1}{R + j\omega L}$$

$$Y_2 = \frac{1}{R + \frac{1}{j\omega C}}$$

So,

$$Y_{eq} = Y_1 + Y_2$$

$$Y_{eq} = \frac{1}{R + j\omega L} + \frac{1}{R + \frac{1}{j\omega C}} \quad \dots(1)$$

$$= \frac{R - j\omega L}{R^2 + (\omega L)^2} + \frac{j\omega C(1 - j\omega RC)}{(1 + jR\omega C)(1 - jR\omega C)}$$

$$\Rightarrow Y_{eq} = \frac{R - j\omega L}{R^2 + (\omega L)^2} + \frac{j\omega C}{1 + \omega^2 R^2 C^2} + \frac{\omega^2 C^2 R}{1 + \omega^2 C^2 R^2}$$

At resonance  $\text{Im}(Y_{eq}) = 0$  (j term of  $Y_{eq}$  will be zero)

$$\Rightarrow \frac{\omega L}{R^2 + \omega^2 L^2} = \frac{\omega C}{1 + \omega^2 R^2 C^2}$$

$$\Rightarrow L + \omega^2 R^2 C^2 L = \omega^2 L^2 C + CR^2$$

$$\Rightarrow L - CR^2 = \omega^2 L^2 C - \omega^2 R^2 C^2 L$$

$$\Rightarrow L - CR^2 = \omega^2 LC(L - CR^2)$$

$$\Rightarrow \omega = \sqrt{\frac{1}{LC}} = \frac{1}{\sqrt{4 \times 4}} = \frac{1}{4} \text{ rad/sec.} \quad \dots(2)$$

At  $\omega = \frac{1}{4}$  rad/sec. from eqn. (1) and (2)

$$Y_{eq} = \frac{1}{2-j1} + \frac{1}{2+j1} = \frac{4}{5} \text{ S} \Rightarrow Z_{eq} = \frac{5}{4} \Omega = R_{eq}$$


$$P = (I_{rms})^2 R_{eq} = \left( \frac{V_{rms}}{R_{eq}} \right)^2 \cdot R_{eq}$$

$$P = \frac{\left( \frac{10}{\sqrt{2}} \right)^2}{\frac{5}{4}} = \frac{100}{2 \times 5} \times 4 = 40 \text{ W}$$

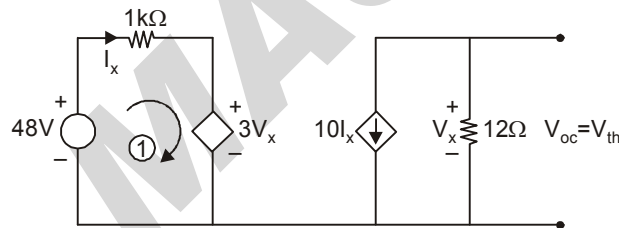56. (a)

First determine thevenin equivalent circuit and then calculate the current through  $24\Omega$  to find the power consumed.

Open circuiting the  $24\Omega$  resistor.



$$V_{th} = -10 I_x \cdot 12 = -120 I_x = V_x \quad \dots(1)$$

But in loop (1)


$$I_x = \frac{48 - 3V_x}{1000} = \frac{48 - 3V_{th}}{1000} \quad \dots(2)$$

On solving equation (1) and (2)

$$V_{th} = -120 \left( \frac{48 - 3V_{th}}{1000} \right)$$

$$V_{th} = -9 \text{ V} = V_{oc}$$

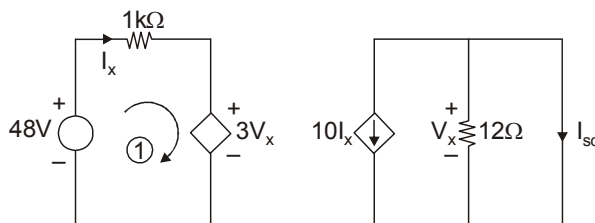Now by short circuiting the  $24\Omega$  resistor




as

$$V_x = 0 \text{ and } I_{sc} = -10 I_x$$

but in loop (1) using KVL equation

$$48 = 1000 \times I_x$$
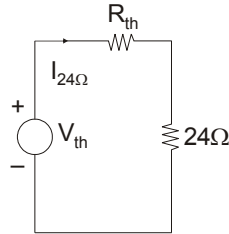
$$\begin{aligned} I_x &= 48 \text{ mA} \\ \Rightarrow I_{sc} &= -480 \text{ mA} \\ \text{Hence } R_{th} &= \frac{V_{th}}{I_{sc}} = \frac{9}{.48} = 18.75 \Omega \end{aligned}$$




$$\begin{aligned} I_{24\Omega} &= \frac{V_{th}}{R_{th} + 24} = \frac{9}{24 + 18.75} \\ I_{24\Omega} &= 0.21 \text{ A} \end{aligned}$$


So power consumed by  $24\Omega = I^2 R = (.21)^2 \times 24 = 1.0584 \text{ w}$

57.

(c)

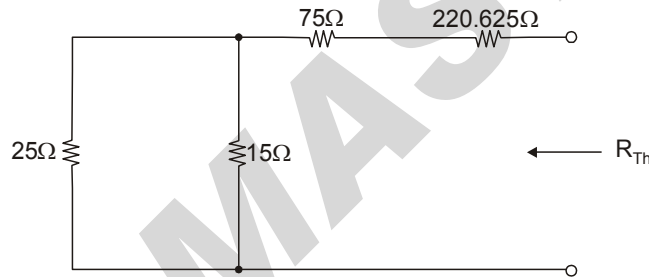To Find  $R_{Th}$ :

$$\begin{aligned} R_{Th} &= (25 \parallel 15) + 75 + 220.625 \\ &= \frac{25 \times 15}{40} + 75 + 220 = 305 \Omega \end{aligned}$$

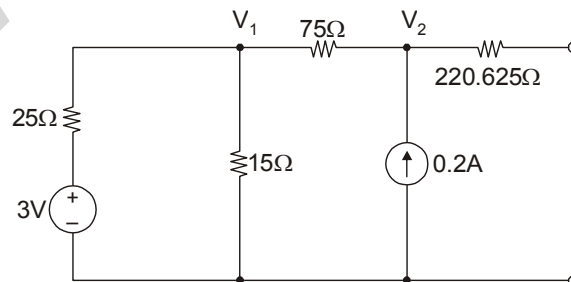To find  $V_{Th}$ :

By KCL

$$\frac{V_1 - 3}{25} + \frac{V_1 - V_2}{75} + \frac{V_1}{15} = 0$$

$$\text{or, } \frac{3V_1 - 9 + V_1 - V_2 + 5V_1}{75} = 0$$

$$\text{or } 9V_1 - V_2 = 9$$

...(1)



Also 
$$\frac{V_2 - V_1}{75} = 0.2$$


or 
$$-V_1 + V_2 = 15 \quad \dots(2)$$

Solving (1) and (2)

$$V_1 = 3V \quad V_2 = 18V$$

$V_{Th} = V_2$  as no current flows in  $220.625\Omega$  resistor.

The equivalent ckt now becomes

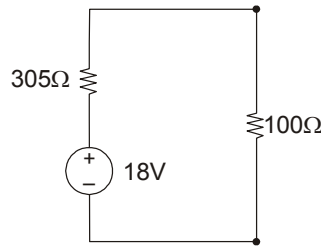


Power delivered to  $100\Omega$  resistor is

$$P = \left( \frac{18}{305 + 100} \right)^2 \times 100$$

$$= 0.19753 \text{ W}$$

or 
$$P = 0.1975 \text{ W [upto power decimal places]}$$

58. (a)

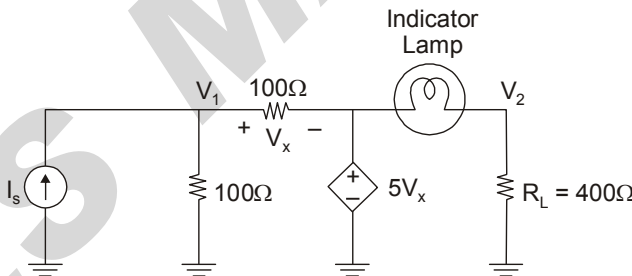

Given, 
$$P_{RL} = 1 \text{ W}$$

$$\therefore P_{RL} = \frac{V_2^2}{400} = 1$$

$$\therefore V_2|_{\max} = 20 \text{ V}$$

For  $V_2 = 20 \text{ V}$

$$I_L = \frac{V_2}{R_L} = \frac{20}{400} = 0.05 \text{ A} < 1\text{A}$$

$\Rightarrow$  resistance of lamp is  $20\Omega$ .

Now, by Nodal analysis

$$\frac{V_1}{100} + \frac{V_1 - 5V_x}{100} = I_s$$

or  $2V_1 - 5V_x = 100I_s$  .....(1)

Also,  $\frac{V_2}{400} + \frac{V_2 - 5V_x}{20} = 0$

$\therefore 21V_2 - 100V_x = 0$  ... (2)

As,  $V_x = V_1 - 5V_x$

$V_x = \frac{V_1}{6}$  ....(3)

Substituting in eqn. (1) and (2)

$2V_1 - \frac{5V_1}{6} = 100 I_s$

or  $7V_1 = 600 I_s$  ... (4)

Similarly,  $21V_2 - \frac{100V_1}{6} = 0$


As  $V_2 = 20 V$

$21 \times 20 - \frac{100V_1}{6} = 0$  ....(5)

From Eqn. (4), we get

$I_s = \frac{7V_1}{600} = \frac{7 \times 25.2}{600} = 0.294 A$

59. (c)

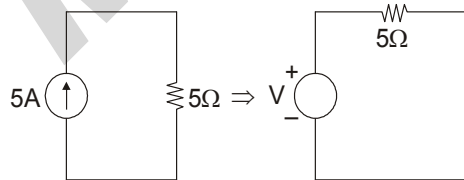


(Using current source to voltage source transformation)

$V = 5 \times 5 = 25 \text{ volt}$

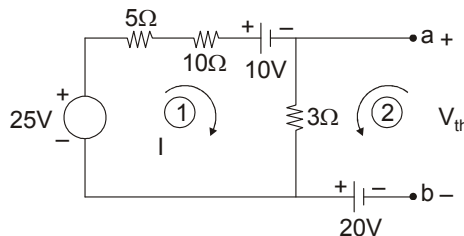**For  $V_{th}$**

$V_{th}$  is the open circuit voltage across ab so equivalent circuit.



Using KVL in loop (1)

$-25 + (5+10+3) I + 10 = 0$


$I = \frac{15}{18} = \frac{5}{6} A$

Using KVL equation in loop (2)

$$\begin{aligned}
 -V_{th} + 3I + 20 &= 0 \\
 V_{th} &= +20 + 3I \\
 &= 20 + \frac{5}{6} \times 3 = 20 + \frac{15}{6} \\
 V_{th} &= 22.5V
 \end{aligned}$$

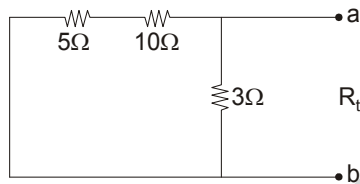**For  $R_{th}$**

By short circuiting the all independent voltage sources & open circuiting independent current source. The equivalent circuit is




$$\begin{aligned}
 R_{th} &= (5 + 10) \parallel 3 \\
 &= 15 \parallel 3 \\
 &= \frac{15 \times 3}{15 + 3} = 2.5\Omega
 \end{aligned}$$

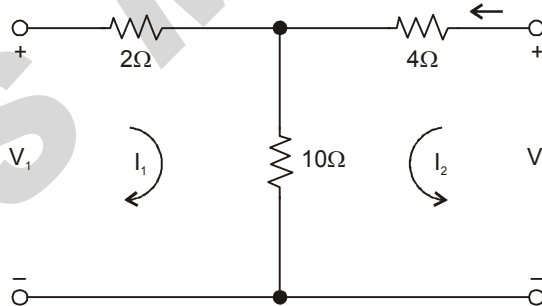60. (c)

By definition of transmission parameters

$$\begin{aligned}
 V_1 &= AV_2 + B(-I_2) \\
 I_1 &= CV_2 + D(-I_2)
 \end{aligned}$$



$$V_1 = 2I_1 + 10(I_1 + I_2) = 12I_1 + 10I_2 \quad \dots(1)$$

$$V_2 = 4I_2 + 10(I_1 + I_2) = 10I_2 + 14I_1 \quad \dots(2)$$

From equation (2)

$$I_1 = \frac{1}{10}(V_2 - 14I_2)$$

$$I_1 = 0.1V_2 - 1.4I_2$$

$$I_1 = 0.1V_2 + 1.4(-I_2) \quad \dots(4)$$

Substituting value of  $I_1$  in eqn. (1)

$$V_1 = 12(0.1V_2 - 1.4I_2) + 10I_2$$

$$V_1 = 1.2V_2 - 6.8I_2$$

$$V_1 = 1.2V_2 + 6.8(-I_2) \quad \dots(5)$$


From eqn. (5) and (4)

$$V_1 = 1.2V_2 + 6.8(-I_2)$$

$$I_1 = 0.1V_1 + 1.4(-I_2)$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1.2 & 6.8 \\ 0.1 & 1.4 \end{bmatrix}$$

61. (d)

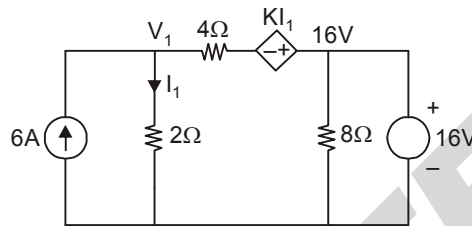

Using node equation at node 1

$$\frac{V_1}{2} + \frac{V_1 - 16 + KI_1}{4} = 6$$

$$\Rightarrow V_1 - 16 + KI_1 + 2V_1 = 24 \quad \therefore V_1 = 2I_1$$

$$\Rightarrow V_1 + \frac{KV_1}{2} + 2V_1 = 16 + 24$$

$$V_1 [2 + K + 4] = 80$$

$$V_1 [6 + K] = 80$$

$$V_1 = \frac{80}{6 + K} \quad \dots(1)$$

Since

$$P_{2\Omega} = 2I_1^2 \leq 50W$$

$$I_1 \leq \sqrt{\frac{50}{2}} \leq 5A$$

$$V_1 = 2I_1$$


$$V_1 \leq 10V \quad \dots(2)$$

from equation (1) and (2)

$$\frac{80}{6 + K} \leq 10V$$

$$\frac{80}{10} \leq 6 + K \Rightarrow K \geq 2$$

62. (a)

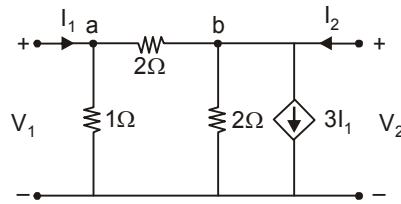

Using KCL equation at node 'a'

$$I_1 = \frac{V_1}{1} + \frac{V_1 - V_2}{2}$$

$$I_1 = V_1(1.5) - .5V_2 \quad \dots(1)$$

Using KCL equation at node 'b'

$$\frac{V_2}{2} + \frac{V_2 - V_1}{2} + 3I_1 - I_2 = 0$$

$$V_2 \left( \frac{1}{2} + \frac{1}{2} \right) - V_1(.5) + 3I_1 - I_2 = 0$$

$$\Rightarrow V_2 - .5V_1 + 3I_1 = I_2 \quad \dots(2)$$

We know

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

as

$$I_2 = 0, \frac{V_1}{I_1} = Z_{11} \text{ and } \frac{V_2}{I_1} = Z_{21}$$

and as

$$I_1 = 0, \frac{V_1}{I_2} = Z_{12} \text{ and } \frac{V_2}{I_2} = Z_{22}$$

Putting  $I_2 = 0$  in equation (2) and putting the value of  $V_2$  in equation (1) we get

$$V_2 = .5V_1 - 3I_1,$$

$$I_1 = V_1(1.5) - .5(5V_1 - 3I_1)$$

$$I_1 = V_1(1.5) - .25V_1 + 3I_1 \times .5$$

$$I_1 = +1.25 V_1 + 1.5 I_1$$

$$-.5 I_1 = 1.25 V_1 = \frac{V_1}{I_1} = \frac{-.5}{1.25} = -.4\Omega$$

Putting value of  $V_1$  in equation (1)

$$\text{We get } \frac{V_2}{I_1} = Z_{21} = -3.2\Omega$$

Put  $I_1 = 0$  in equation (1) and (2)


Put  $V_1$  in equation (2)

$$V_1 = \frac{1}{3}V_2, I_2 = (V_2)\left(\frac{1}{2} + \frac{1}{3}\right) = \frac{5}{6}V_2$$

$$\Rightarrow \frac{V_2}{I_2} = Z_{22} = \frac{6}{5}\Omega$$

$$Z_{12} = \left(\frac{1}{3}\right)\left(\frac{6}{5}\right) = .4\Omega$$

63. (b)

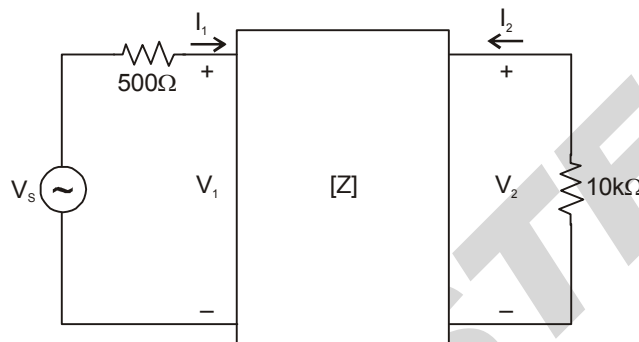

Equation for the two-port are

$$V_1 = 10^3 I_1 + 10I_2 \quad \dots(1)$$

$$V_2 = -10^6 I_1 + 10^4 I_2 \quad \dots(2)$$

The characterizing equations of the input and output networks are

$$V_s = 500 I_1 + V_1 \quad \dots(3)$$

$$V_2 = -10^4 I_2 \quad \dots(4)$$

Substituting  $V_2$  in eqn. (2)

$$-10^4 I_2 = -10^6 I_1 + 10^4 I_2$$


or

$$I_2 = \frac{10^6}{2 \times 10^4} I_1 = 50 I_1 \quad \dots(5)$$

$$\frac{I_2}{I_1} = 50$$

64. (b)

Considering section A

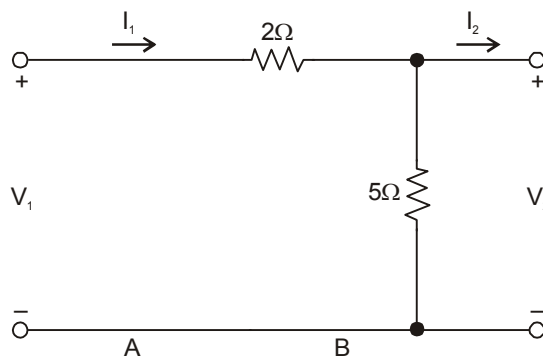

$$V_1 = 2I_1 + V_2 \quad \dots(1)$$

$$I_2 = \frac{V_2}{5} + I_1 = -0.2V_2 + I_1 \quad \dots(2)$$

From eqn. (2)

$$I_1 = +0.2V_2 + I_2 \quad \dots(3)$$

Substituting in eqn. (1)

$$V_1 = 2(+0.2V_2 + I_2) + V_2$$


or

$$V_1 = 1.4V_2 + 2I_2 \quad \dots(4)$$

From eqn. (3) and (4)

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} = \begin{bmatrix} 1.4 & 2 \\ 0.2 & 1 \end{bmatrix}$$

Similarly for network B

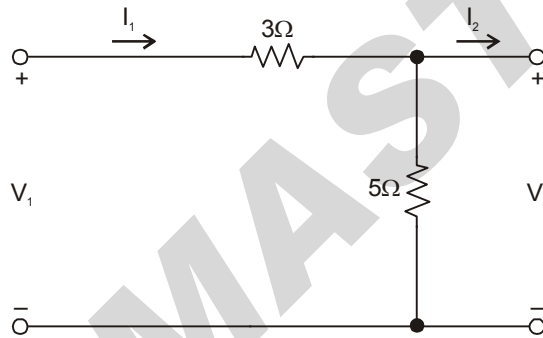

$$V_1 = 3I_1 + V_2 \text{ and } I_2 = -\frac{V_2}{5} + I_1$$

$$\therefore I_1 = I_2 + 0.2V_2 = 0.2V_2 + I_2$$

$$\therefore V_1 = 3(I_2 + 0.2V_2) + V_2 = 1.6V_2 + 3I_2$$

Therefore,  $\begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} = \begin{bmatrix} 1.6 & 3 \\ 0.2 & 1 \end{bmatrix}$

The equivalent ABCD matrix

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1.4 & 2 \\ 0.2 & 1 \end{bmatrix} \begin{bmatrix} 1.6 & 3 \\ 0.2 & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2.64 & 6.2 \\ 0.52 & 1.6 \end{bmatrix}$$

65. (c)

For the two-port network

$$[Y] = \begin{bmatrix} 0.005 & -0.004 \\ 0.05 & 0.03 \end{bmatrix}$$

Therefore,

$$I_1 = 0.005V_1 - 0.004V_2 \quad \dots(1)$$

$$I_2 = 0.05V_1 + 0.03V_2 \quad \dots(2)$$

$$\frac{100 - V_1}{R_s} = I_1 \quad \dots(3)$$

$$\therefore \frac{100 - V_1}{25} = 0.005V_1 - 0.004V_2$$

or  $100 = 1.125V_1 - 0.1V_2 \quad \dots(4)$

Also,  $I_2 = -\frac{V_2}{R_L} = -\frac{V_2}{100} \quad \dots(5)$

$$\therefore -\frac{V_2}{100} = 0.05V_1 + 0.03V_2$$

or  $0.05V_1 + 0.04V_2 = 0 \quad \dots(6)$

From eqn. (6),  $V_2 = -\frac{5}{4}V_1$  so eqn. (4) becomes

$$100 = 1.125V_1 - 0.1\left(-\frac{5}{4}V_1\right)$$

or  $V_1 = \frac{100}{1.25} = 80 \text{ V}$