

Assistant Engineer Prelims Exam Electrical Engineering Paper-II

UPPSC 2020

**Detailed Solution (SET-C)** 

Exam Date - 13<sup>th</sup> December Time - 02:00 PM - 04:30 PM

Office Address: F-126, Katwaria Sarai, New Delhi - 110 016 Telephone: 011-41013406, Mobile: 8130909220, 9711853908



## SET - C

- 1. While deciding any question relating to the 6. disqualification of a member of parliament, the president shall obtain the opinion of (a) Election justice of India (b) Chief Justice of India (c) Attorney General (d) Speaker of the lok Sabha Ans. (a) 2. Soyabean seed contains (a) 20% protection and 40% oil (b) 40% protein and 10% oil (c) 40% protein and 20% oil (d) 20% protein and 20% oil Ans. (c) 3. As per the results of 'Swachh Sarvekshan' 2020', announced by Ministry of Housing and Urban Affairs on 20<sup>th</sup> August 2020, Which is the Cleanest City in Uttar Pradesh? (a) Agra (b) Gaziabad (c) Lucknow (d) Prayagraj Ans. (c) 7. 4. How many teachers from Uttar Pradesh were select for 'National Award' on Teachers day 5<sup>th</sup> Sept., 2020? (b) Five (a) Six Ans. (c) (c) Four (d) Three 8. Ans. (d) 5. 'Poshan Maah' was celebrated by Government of India in the year 2010, in which of the following months? (a) September (b) August (c) July (d) June
- Ans. (a)

Match List-I with List-II and choose the correct answer using the code given below.

#### List-I (Text)

- A. Kiratarjuniyam
- B. Dashakumar Charitam
- C. Buddha Charitam
- D. Vikramorvashiyam

#### List-II (Writer)

- A. Dandi
- B. Kalidas
- C. Bharavi
- D. Ashvaghosha

#### Code:

- ABCD
- 1 2 (a) 3 4
- (b) 3 1 4 2
- (c) 2 1 4 3
- (d) 1 3 2 4
- Ans. (b)
- A large tank near Mohoba, temples at Ajaygarh and Mahoba and city of Rajavansini
  - (a) Nannuk (b) Vakapati
  - (c) Rahil (d) Jayashakt
- Which of the following Rights a cultivator enjoyed on his own land during the Mughal period?
  - (a) Right to mortagage only
  - (b) Right to sell and gift
  - (c) Right to mortgage and gift
  - (d) All the above rights

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



#### Ans. (a)

**9.** Match List-I with List-II and select the correct answer using the code given below.

ES MASTER

Institute for Engineers (IES/GATE/PSUs)

#### List-l

- A. Nokrek
- B. Agasthyamalai
- C. Nandadevi
- D. Dehang Debang

#### List-II

- A. Uttrarakhand
- B. Arunachal Pradesh
- C. Kerala
- D. Meghalya

#### Code:

|     | Α | В | С | D |  |
|-----|---|---|---|---|--|
| (a) | 4 | 3 | 1 | 2 |  |
| (b) | 4 | 3 | 2 | 1 |  |
| (c) | 3 | 4 | 1 | 2 |  |
| (d) | 2 | 3 | 4 | 1 |  |

#### Ans. (a)

**10.** Match List-I with List-II and select the correct answer using the code given below.

#### List-I (Tribes)

- A. Tharus
- B. Todas
- C. Santhal
- D. Gond List-II
- A. Madhya Pradesh
- B. Jharkhand
- C. Uttrarakhand
- D. Tamil Nadu

#### Code:

ABCD

(a) 1 3 4 2

- (b) 4 2 1 3
- (c) 2 1 3 4
- (d) 3 4 2 1

#### Ans. (d)

- 11. State get share of the revenue from
  - (a) Income Tax
  - (b) Customes Revenue
  - (c) Exercise Tax
  - (d) Surcharge on Income Tax

#### Ans. (c)

- **12.** Which Article of the Indian Constitution empowers Parliament to make law for implementing international agreements?
  - (a) Article 249 (b) Article 250
  - (c) Article 252 (d) Article 253

#### Ans. (d)

- **13.** Who appoints the acting Chief Justice of India?
  - (a) Chief Justice of India
  - (b) Chief Justice of India with previous consent of the President
  - (c) President of India
  - (d) President in consulation with the Chief Justice of India
- Ans. (c)
- 14. The rotation intensity of Maize-mustard-mung crop is
  - (a) 100% (b) 200%
  - (c) 300% (d) 400%

#### Ans. (c)

- 15. Which of the following is NOT a kharif crop?
  - (a) Soyabean (b) Lentil
  - (c) Cotton (d) Pigeon pea
- Ans. (b)

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



| 16.  | 'Five Star Vil<br>Government o<br>relates to which | Ilage Scheme' started by<br>f India in September 2020<br>n one of the following? | 21. |
|------|--|--|-----|
|      | (a) Electricity s                                  | upply  |     |
|      | (b) Postal Serv                                    | rices Schemes  |     |
|      | (c) Health Serv                                    | vices  |     |
|      | (d) Primary Ed                                     | ucation  |     |
| Ans. | (b)  |  | Ans |
| 17.  | Which won the Singles Title on                     | US open 2020, Mens Tennis<br>14 <sup>th</sup> September, 2020?                   | 22. |
|      | (a) Alex Zverev                                    | (b) Dominic Thiem  |     |
|      | (c) D.Medvede                                      | v (d) P.C Busta  |     |
| Ans. | (b)  |  |     |
| 18.  | Which of the fo matched?                           | llowing pairs is NOT correctly   |     |
|      | Ancient na<br>of the Citie                         | me Modern name<br>es of the Cities   |     |
|      | (a) Esipattan                                      | Saranath   |     |
|      | (b) Dashapur                                       | Mandsor  |     |
|      | (c) Bansvasi                                       | Talkad   |     |
|      | (d) Mohoday  | Kannauj  |     |
| Ans. | (c)  |  |     |
| 19.  | The early farmine<br>lake is                       | ng site located on the bank of   |     |
|      | (a) Mehargarh                                      | (b) Lahuradeva   |     |
|      | (c) Chirand  | (d) T-Narsipur   |     |
| Ans. | (d)  |  | Ans |
| 20.  | Author of the discussisses at was                  | 'Dastane Mazahib' which<br>bout the Din-i Ilahi of akbar,                        | 23. |
|      | (a) Mohammac                                       | l Rabbanj  |     |
|      | (b) Mohasin Fa                                     | aani   |     |
|      | (c) Badauni  |  |     |
|      | (d) Afif   |  |     |
| Ans. | (b)  |  | Ans |

- Who was appointed the minister of 'Minster of Rehabilitation' set up on 06 September, 1947?
  - (a) S.P Mukerj
  - (b) Sardar Vallabhabhai Patel
  - (c) J.L Nehru
  - (d) K.C Niyogi

#### Ans. (d)

2. Match List-I with List-II and select the correct answer using the code given below.

#### List-I (States)

- A. Tamil Nadu
- B. Rajasthan
- C. Nagaland
- D. Madhya Pradesh List-II (Highest Peaks)
- A. Dhoopgarh
- B. Saramati
- C. Guru Shikhar
- D. Doda Betta

#### Code:

|     | Α | В | С | D |
|-----|---|---|---|---|
| (a) | 3 | 4 | 1 | 2 |
| (b) | 1 | 2 | 4 | 3 |
| (C) | 4 | 3 | 2 | 1 |
| (d) | 2 | 1 | 3 | 4 |

#### Ans. (c)

- 23. 'Leopold Matrix' is associated with
  - (a) Weather Forecasting
  - (b) Disaster Management
  - (c) Environmental Impact Assessment Method
  - (d) Environmental Law
- Ans. (c)

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org





## ES MASTER

Institute for Engineers (IES/GATE/PSUs)

- 24. The joint Sitting of the Indian Parliament for transacting a legislative business is president over by
  - (a) The President of India
  - (b) The senior most Member of Parliament
  - (c) The Chairman of the Rajya Sabha
  - (d) The speaker of the Lok Sabha
- Ans. (d)
- 25. The term 'Office of Profit' has been defined by the
  - (a) Consitution
  - (b) Parliament
  - (c) Supreme Court
  - (d) Union Council of Minsters

#### Ans. (b)

- 26. Consider the following statements related to induction motor drives:
  - 1. Power to weight ratio is high
  - 2. Suitable for operation at high voltage
  - 3. Suitable for high speed operation.
  - 4. Power converter is simple and economical.
  - 5. Speed control is easy and of low cost.
  - 6. Reliability is good

Out of these statements

- (a) 1, 2, 4 and 6 are correct
- (b) 2, 3, 5 and 6 are correct
- (c) 1, 2, 3 and 5 are correct
- (d) 1, 2, 3 and 6 are correct

Ans. (d)

- 27. In constant V/F speed control of a 3-phase induction motor, if frequency is increased from low value to the rated value, the maximum torque  $(T_{max})$  and slip corresponding to the maximum torque (S<sub>m</sub>) varies as
  - (a) T<sub>max</sub> increases, S<sub>m</sub> decreases

- **UPPSC-AE-2020 Detailed Solution Electrical Engineering-II**
- (b) T<sub>max</sub> increases, S<sub>m</sub> Increases
- (c) T<sub>max</sub> constant, S<sub>m</sub> decreases
- (d)  $T_{max}$  constant  $S_m$  increases
- Ans. (C)

Sol. 
$$S_{max} = \frac{R'_2}{X'_2}$$
  
 $S_{max} \propto \frac{1}{f}$   
 $T = \frac{3V^2}{2\omega_{sm}X'_2}$  (:: V \infty f)

- T = frequency independent
- 28. The drive has following equations of motor and load torques in terms of speed

$$T = \frac{2}{\omega} + 2, T_{L} = \frac{4}{\omega}$$

The equilibrium point is

- (a) Unstable
- (b) Stable
- (c) Marginally
- (d) Nothing can be said
- Ans. (b)
- 29. In a non-circulating current mode dual converts, the circulating current is avoided by
  - (a) Connecting a series reactor
  - (b) Maintaing  $\alpha_1 + \alpha_2 = 180^\circ$
  - (c) Operating only converter
  - (d) Adding an extra SCR
- Ans. (c)
- 30. An SCR is made up of silicon because
  - (a) Silicon has larger leakage current than germanium
  - (b) Silicon has small leakage current than germanium
  - (c) Silicon has small leakage voltage than germanium

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org

## GATE 2021 Full-Length Test Series

### CE|ME|EE|ECE

Starts from **20<sup>th</sup> Dec** 



## **6 Full-Length Tests**

### @ **₹300/- + GST**

- Matches level & orientation of GATE
- Thoroughly researched test papers

**ENROLL NOW** 



F-126, Katwaria Sarai, New Delhi-110016 | Call +91 801 00 09955 Email: info@iesmaster.org



Ā

(d) Silicon has larger leakage voltage than germanium

#### Ans. (b)

- **31.** For an application which requires smooth and precise control over the wide range at low cost, the motor preferred is
  - (a) Squirrel cage induction motor
  - (b) Synchronous motor
  - (c) D.C motor
  - (d) Wound rotor induction motor

#### Ans. (c)

- **32.** In adjustable frequency 3-phase induction motor drives, for constant power application the slip speed is kept
  - (a) Constant
  - (b) Proportional to synchornous speed
  - (c) Inversely proportional to synchronous speed
  - (d) Proportional to square of synchronous speed

#### Ans. (a)

- **33.** The output of logic gate is 1 when all of its input are at logic 0. The gate is either
  - (a) a NAND or an EX-OR
  - (b) a OR or an EX-NOR
  - (c) an AND or an EX-OR
  - (d) a NOR or an EX-NOR

#### Ans. (d)

- 34. Hamming code is capable of
  - (a) Only detects single bit error
  - (b) Only corrects single bit error
  - (c) Detects and corrects single bit error
  - (d) None of the above
- Ans. (c)

(a) J = K (b) J = K = 1

(c) 
$$J = 0$$
,  $K = 1$  (d)  $J =$ 

#### Ans. (d)

- **36.** The complement of  $\left[ (A \cdot \overline{B} + \overline{C}) \cdot D + \overline{E} \right] \cdot F$  is
  - (a)  $\left[ (A + \overline{B}) \cdot \overline{C} + D \cdot \overline{E} \right] + F$
  - (b)  $\left[\left(\overline{A}+B\right),\overline{C}+D+\overline{E}\right]$ .F
  - (c)  $\left[ (\overline{A} + B) \cdot C + \overline{D} \right] \cdot E + \overline{F}$
  - (d)  $\left[ (A + \overline{B}) \cdot C + \overline{D} \right] \cdot \overline{E} + F$

#### Ans. (c)

- Sol. Component of function :
  - $= \overline{\left[ (A \cdot \overline{B} + \overline{C}) \cdot D + \overline{E} \right] \cdot F}$
  - $= \overline{\left[ (A \cdot \overline{B} + \overline{C}) \cdot D + \overline{E} \right]} + \overline{F}$
  - =  $\overline{\left[(A \cdot \overline{B} + \overline{C}) \cdot D\right]} \cdot E + \overline{F}$
  - $= \left( \overline{(A \cdot \overline{B}) + \overline{C}} + \overline{D} \right) \cdot E + \overline{F}$
  - $= ((\overline{A \cdot \overline{B}}) \cdot C + \overline{D}) \cdot E + \overline{F}$
  - $= ((\overline{A} + B) \cdot C + \overline{D}) \cdot E + \overline{F}$
- **37.** A combination circuit has inputs A, B and C, its K-map is given below. The output of circuit is given by



**35.** A D-flip-flop can be made from a J-K flip-flop by making

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



#### 

MAS

Institute for Engineers (IES/GATE/PSUs)



Output =  $A \oplus B \oplus C$ 

**38.** Find out the integrating type analog to digital converter from the following.

- (a) flash type converter
- (b) tracking converter
- (c) successive approximation type converter
- (d) dual-slope analog to digital converter

#### Ans. (d)

- **39.** The minimum number of 2-input NAND gates required to realize the logic function  $Y = A\overline{B} + \overline{A}B$  is
  - (a) 5 (b) 3
  - (c) 6 (d) 4
- Ans. (d)

**Sol.**  $y = A\overline{B} + \overline{A}B = A \oplus B$ 



4 NAND gate require

- 40. Find the cut-off frequency for an RC low pass filter of R =  $8.2\Omega$  and C = 0.0033  $\mu$ F.
  - (a) 6 kHz (b) 5.88 kHz
  - (c) 4.26 kHz (d) 7.91 kHz
- Ans. (\*)
- Sol. Cut of frequency

$$f_{c} = \frac{1}{2\pi RC}$$
$$f_{c} = \frac{1}{2\pi \times 8.2 \times 0.0033 \times 10^{-6}}$$

#### UPPSC-AE-2020 Detailed Solution Electrical Engineering-II

$$= \frac{10^6}{0.1699} = 5.88 \text{ MHz}$$

- **41.** Why synchronous transmission is preferred more?
  - (a) it has no start and stop bit
  - (b) it is cheaper than asynchronous
  - (c) it is easier to implement
  - (d) less complex

#### Ans. (a)

- **Sol.** In synchronous transmission both sender and receiver access the data according to same clock. It has no start & stop bits & thus it has more efficient.
- **42.** A 400 W carrier is amplitude modulated with m = 0.75. The total power in AM is
  - (a) 400 W (b) 512 W
  - (c) 588 W (d) 650 W

Ans. (b)

Sol.

$$P = P_{c} \left( 1 + \frac{m^{2}}{2} \right)$$
$$= 400 \left[ 1 + \frac{(0.75)^{2}}{2} \right]$$
$$= 512.5 W$$

**43.** An air filled rectangular waveguide has inner dimensions of 3cm × 2cm. The wave impedance of the TE<sub>20</sub> mode of propagation in the waveguide at a frequency of 30 GHz is \_\_\_\_\_\_. (free space impedance  $\eta_0 = 377 \Omega$ )

| (a) 30802 (b) 3550 | (a) 30 | 08Ω | (b) | 355Ω |
|--------------------|--------|-----|-----|------|
|--------------------|--------|-----|-----|------|

(c)  $400\Omega$  (d)  $461\Omega$ 

Ans. (c)

**Sol.** Inner dimension of waveguide in 3cm × 2cm free space impedance,  $\eta_0 = 377\Omega$ 

Wave impedance  $\eta\,$  for the  ${\sf TE}_{20}$  mode at f =

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



30 GHz is given by

$$\eta = \frac{\eta_0}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

$$C = \frac{C}{\sqrt{2}} = \frac{C}{2} + \frac{3 \times 10^8}{2}$$

$$f_c \text{ for } TE_{20} = \frac{C}{2} \sqrt{\left(\frac{2}{3}\right)^2} + 0 = \frac{C}{2} \times \frac{2}{3} = \frac{3 \times 10^6}{3}$$

 $f_c = 10 \text{ GHz}$ 

So, 
$$\eta = \frac{377}{\sqrt{1 - \left(\frac{10}{30}\right)^2}} = \frac{377}{0.943} \approx 400 \,\Omega$$

**44.** Noise temperature of Sun is more than \_\_\_\_\_K.

| (a) | 1000   | (b) | 5000 |
|-----|--------|-----|------|
| (a) | 100000 | (d) | 500  |

(c) 100000 (d) 500

Ans. (c)

- **45.** A cavity magnetron uses strapping to
  - (a) prevent mode jumping
  - (b) precevent cathode back heating
  - (c) ensure bunching
  - (d) improve the phase focussing effect

#### Ans. (a)

- **46.** A microwave tube amplifier uses an axial magnetic field and a radial electric field. This is a
  - (a) Reflex klystron
  - (b) Co-axial magnetron
  - (c) Travelling wave magnetron
  - (d) CFA

Ans. (d)

- **Sol.** CFA  $\rightarrow$  Cross field amplifier
- **47.** In a circular waveguide, the dominated mode is
  - (a)  $TE_{01}$  (b)  $TE_{11}$ (c)  $TE_{20}$  (d)  $TE_{21}$

#### Ans. (b)

- A hollow rectangular waveguide can NOT propagate TEM wave because
  - (a) Of the existance of only one conductor
  - (b) Of the losses caused
  - (c) It is dependent on the type of the material used
  - (d) None of the above

#### Ans. (a)

- **49.** The most commonly used method for the protection of three phase feeder is
  - (a) Time graded protection
  - (b) Differential protection
  - (c) Reverse power protection
  - (d) None of these
- Ans. (b)
- **50.** Discrimination between main and backup protection is provided by the use of relays which are
  - (a) Fact (b) Scrisitive
  - (c) Slow (d) None of these

#### Ans. (c)

- 51. Which of the following statements is correct?
  - (a) Station batteries are used to operate relay only
  - (b) The lightning arrestors have surge divertors
  - (c) An impedance relay has maximum fault current near the relay
  - (d) A high speed relay has an operation of 1-2 cycles
- Ans. (b)
- **52.** With the use of high speed circuit breakers, which among the following stability is increased?
  - (a) Steady-state stability

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



- (b) Transient stability
- (c) Frequency stability
- (d) All of the above
- Ans. (b)
- **53.** The arcing contacts in a circuit breaker is made of

ES MASTER

Institute for Engineers (IES/GATE/PSUs)

- (a) Copper tungsten alloy
- (b) Porcelain
- (c) Electrolytic copper
- (d) Aluminium alloy

#### Ans. (a)

**54.** A shunt reactor at 100 MVAr is operated at 98% of its rated voltage and at 96% of its rated frequency. The reactive power absorbed by reactor is

| (a) 98 MVAr | (b) 104.02 MVAr |
|-------------|-----------------|
|-------------|-----------------|

- (c) 96.04 MVAr (d) 100.04 MVAr
- Ans. (d)
- **Sol.** (Reactive power)<sub>1</sub> =  $\frac{V^2}{X_s}$  = 100 MVA<sub>r</sub>

(Reactive power)<sub>2</sub> =  $\frac{(0.98)^2 V^2}{0.96 X_S}$ 

= 100.04 MVAr

- **55.** Protective relays can be designed to respond to
  - (a) Light intensity, impedance
  - (b) Temperature, resistance, reactance
  - (c) Voltage and current
  - (d) All of these

Ans. (d)

- **56.** Which one of the following methods used for solution of ordinary differential equations is conditionally stable?
  - (a) Euler's method
  - (b) Milne's method

- (c) Taylor's series method
- (d) Adams-Bashforth method
- Ans. (a)
- **57.** Which one of the following methods used for solving non-linear algebraic equations has rate of convergence 2.0?
  - (a) Bisection method
  - (b) Secant method
  - (c) Newton-Raphson method
  - (d) Muller's method

#### Ans. (b)

- **58.** Which one of the following methods is NOT used for solution of non-linear algebraic equations?
  - (a) Regula-Falsi Method
  - (b) Milne's-Predictor-Corrector Method
  - (c) Secant Method
  - (d) Bisection Method

#### Ans. (b)

#### 59. In a Triclinic crystal, a lattice plane makes

intercepts at a length a, 2b and  $-\frac{3c}{2}$ . The Miller indices of the plane are

- (a) 3 : 6 : 4 (b) 6 : 3 : 4
- (c) 6 : 3 : -4 (d) 6 : 3 : -2

Ans. (d)

| Sol. | Intercept                 | a : 2b : $-\frac{3C}{2}$     |
|------|---------------------------|------------------------------|
|      | Coefficient of intercepts | $1:2:-\frac{3}{2}$           |
|      | Reverse the coefficient   | $1:\frac{1}{2}:-\frac{2}{3}$ |
|      | Miller indices            | 6:3: <b>-</b> 2              |
|      |                           |                              |

**60.** The critical field needed to destroy super conductivity, is known as

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



# **ESE 2021** Prelims Online Test Series

- Covers entire syllabus as per UPSC pattern
- Train your brain & body to face real exam
- Develop consistency in your preparation
- Get comparative performance analysis
- Transform your weakness into strength

GS & Engineering Aptitude (Paper-I) - 32 Tests

Engineering Discipline Technical (Paper-II) - 28 Tests Total 60 Tests CE

ME

EE

ECE

Registrations Open, Enrol Now

To register, visit iesmaster.org or contact IES MASTER help desk at 80100 09955, 97118 53908

(a) 
$$H_o (T_c/T_)$$
 (b)  $H_o (T/T_c)^2$   
(c)  $H_o \left[ 1 - \left( \frac{T_o}{T_c} \right)^2 \right]$  (d)  $H_o \left[ 1 - \left( \frac{T_c}{T_o} \right)^2 \right]$ 

ES MASTER

Institute for Engineers (IES/GATE/PSUs)

Ans. (c)

**Sol.**  $H_{\rm C} = H_{\rm o} \left[ 1 - \left( \frac{T_{\rm o}}{T_{\rm C}} \right)^2 \right]$ 

- **61.** The instruction for startign the computer are housed in
  - (a) Random Access Memory
  - (b) CD ROM
  - (c) Read Only Memory Chip
  - (d) All of the above

Ans. (c)

- **62.** When memory write or I/O read are active, data remains \_\_\_\_\_ of the processor.
  - (a) Input (b) Output
  - (c) Processor (d) None of these
- Ans. (b)
- **63.** While performing read operation, one must taken care that much current should NOT be
  - (a) Sourced from data lines
  - (b) Sinked from data lines
  - (c) Sourced or sinked from data lines
  - (d) Sinked from address lines
- Ans. (c)
- **64.** A three phase induction motor has shaft output of 16 kW. The constant losses are 1 kW. If the slip be 4%, the rotor copper losses would be
  - (a) 600 W (b) 625 W
  - (c) 667 W (d) 720 W
- Ans. (c)

Sol. I.M. shaft output = 16 kW

Copper losses = 
$$\frac{s}{(1-s)} \times P_d$$

 $= \frac{0.04}{(1-0.04)} \times 16 = 667W$ 

- **65.** In a three stack 12/8 pole variable reluctance motor, rotor pole pitch is
  - (a) 15° (b) 30°
  - (c)  $45^{\circ}$  (d)  $60^{\circ}$

#### Ans. (a)

- **66.** The condition of a three phase induction motor at no-load resembles those of a transformer whose secondary
  - (a) Short circuited
  - (b) Open circuited
  - (c) Supplying a variable resistive load
  - (d) Supplying an inductive load
- Ans. (b)
- **Sol.** The operation of an induction motor under the no-load condition is similar to a transformer under open circuit conditon.
  - Similarly, a three phase induction motor with its rotor blocked behaves similarly to a transformer under short circuit conditon.
- **67.** The torque angle  $\delta'$  is the angle between
  - (a) Rotor field axis and resultant field axis
  - (b) Stator field axis and rotor field axis
  - (c) Stator field axis and mutual field axis
  - (d) Stator field axis and resultant field axis

#### Ans. (b)

- **Sol.** Torque angle S is the angle between rotor flux & stator flux.
- **68.** In case of the air gap in an induction motor is increased
  - (a) The magnetizing current of the rotor will decrease

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



- (b) The power factor will decrease
- (c) The speed of motor will increase

ES MASTER

Institute for Engineers (IES/GATE/PSUs)

- (d) The windage losses will increase
- Ans. (b)
- **69.** A stepper motor having a resoltuion of 300 steps/revolution and runnign at 2400 rpm has a pulse rate of \_\_\_\_pps.
  - (a) 4000 (b) 8000
  - (c) 6000 (d) 10000
- Ans. (c)
- **70.** A 3-phase, 6-pole, 50 Hz, squirrel cage induction motor is runnign at a slip of 5%. The speed of stator magnetic field to rotor magnetic field and speed of rotor with respect to stator magnetic field are
  - (a) Zero, 50 rpm
  - (b) Zero, 955 rpm
  - (c) 1000 rpm, 50 rpm
  - (d) 1000 rpm, 955 rpm

Ans. (a)

- Sol.
- The speed of stator magnetic field to rotor magnetic field is zero, because both field rotating at synchronous speed.
- Speed of rotor with respect to stator magnetic field = SN<sub>s</sub>

$$= 0.05 \times \frac{120 \times 50}{6}$$
  
= 50

- **71.** In a commutation circuit used to turn-off an SCR, satisfactory turn-off is obtained, when
  - (a) Circuit turn-off time < device turn-off time
  - (b) Circuit turn-off time > device turn-off time
  - (c) Circuit time constant > device turn-off time
  - (d) Circuit time constant < device turn-off time
- Ans. (b)

- 72. A TRIAC is a
  - (a) 2-terminal switch
  - (b) 2-terminal bilateral switch
  - (c) 3-terminal unidirectional switch
  - (d) 3-terminal bidirectional switch
- Ans. (d)
- **73.** Two thyristors of same rating and same specifications
  - (a) Will have equal turn-on and turn-off periods
  - (b) Will have equal turn-on, but unequal turnoff periods
  - (c) May have equal or unequal turn-on and turn-off periods
  - (d) Will have unequal turn-on and turn-off periods
- Ans. (c)
- **74. Assertion (A):** Inverter and choppers use fast switching thyristors.

Reason (R): Fast switching SCR has low turnoff time

- (a) Both (A) and (R) are correct and (R) is the correct explanation of (A)
- (b) Both (A) and (R) are correct but (R) is not the correct explanation of (A)
- (c) (A) is correct but (R) is wrong
- (d) (A) is wrong but (R) is correct
- Ans. (a)
- **75.** In a single phase fully controlled bridge rectifier, the output load current I is ripple free. The r.m.s. value of source current would be
  - (a)  $2\sqrt{2} I/\pi$  (b) I
  - (c) I/2 (d) I/4

Ans. (b)

Sol. Single phase fully controlled bridge rectifier

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



(d) None of above



MAS

Institute for Engineers (IES/GATE/PSUs)

r.m.s value of source wave form is I

**76.** Consider the following statements related to dc drives:

- 1. Wide speed control range
- 2. High starting torque
- 3. High power to weight ratio
- 4. Fast transient response
- 5. No limit on highest operating voltage
- Out of these statements
- (a) 1, 2 and 3 are correct
- (b) 2, 3, and 4 are correct
- (c) 1, 2 and 4 are correct
- (d) 3, 4 and 5 are correct
- Ans. (c)
- 77. A 20 kW electric motor has heating time constant 60 min. Iron loss is equal to full load copper loss. The short time rating of the motor for 15 minute is

- (a) 43.5 kW (b) 56.7 kW
- (c) 60.0 kW
- Ans. (c)
- 78. A 220 V, 20 A, 1000 rpm, separately excited d.c. motor has armature resistance of 1 ohm. The motor is supplied from 250 V dc supply via a step down chopper, for operation of motor at 500 rpm at the rated torque, the duty ratio of the chopper should be
  - (a) 0.40 (b) 0.44
  - (c) 0.48 (d) 0.50
- Ans. (a)
- Sol. For motor

$$E_{b} = V - I_{a}R_{a}$$
  
= 220 - 20 × 1 = 200

Rated torque

$$\tau_{\text{rated}} = \frac{200 \times 20}{2\pi \times 1000} \times 60$$
$$= 38.2165 \text{ N-m}$$

Now motor supplied from 250 V dc supply via a step down chopper

 $E_{b_2} = 250\alpha - 20$ 

Here  $\alpha \rightarrow$  duty ratio

motor at 500 rpm at the rated torque (rated current)

$$38.2165 = \frac{(250\alpha - 20) \times 20}{2\pi \times 500} \times 60$$

 $\alpha = 0.48$ 

- **79.** The consideration involved in the selection of the type of electric drive for a specific application depends upon
  - (a) Speed control range and its nature
  - (b) Starting nature
  - (c) Environmental condition
  - (d) All the above

Ans. (d)

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



- **80.** A single phase half-wave rectifier circuit has free-wheeling diode, the free-wheeling diode will conduct only if
  - (a) load is purely resistive
  - (b) load is purely inductive
  - (c) load is combination of R and L
  - (d) load is purely inductive or combination of R and L

Ans. (d)

81. Find the expression for peak capacitor voltage in case of current commuted chopper circuit.

(a) 
$$I_o \sqrt{\frac{L}{C}}$$
 (b)  $V_s + \sqrt{\frac{L}{C}}$   
(c)  $V_s + I_o \sqrt{\frac{L}{C}}$  (d) O (Zero)

Ans. (c)

- **82.** Which one of the following is NOT inherently constant torque motor?
  - (a) DC series motor
  - (b) DC shunt motor
  - (c) Three phase induction motor
  - (d) Single phase induction motor

#### Ans. (a)

- 83. A 4-bit R/2R digital to analog converter (DAC) has a reference of 5 Volts. What is the analog output for input code 0101?
  - (a) 0.3125 V (b) 3.125 V
  - (c) 0.78125 V (d) -3.125 V

Ans. (d)

**Sol.**  $V_o = -\frac{V_r}{2^{n-1}}$  (Decimal equivalent of binary

number)

$$= -\frac{5}{8}(5) = -3.125$$

**84.** Which of the following equations satisfy the J-K flip-flop?

#### UPPSC-AE-2020 Detailed Solution Electrical Engineering-II

- (a)  $Q_{n+1} = J_n \overline{Q}_n + \overline{K}_n Q_n$
- (b)  $Q_{n+1} = \overline{J}_n \overline{Q}_n + K_n Q_n$
- (c)  $Q_{n+1} = J_nQ_n + K_nQ_n$
- (d)  $Q_{n+1} = \overline{J}_n \overline{Q}_n + \overline{K}_n \overline{Q}_n$
- Ans. (a)

**Sol.** 
$$Q_{n+1} = J_n \overline{Q}_n + \overline{k}_n Q_n$$

- **85.** POS form of Boolean expression is suitable for circuit implementation, using
  - (a) XOR (b) NAND
  - (c) AND (d) NOR

Ans. (d)

**86.** The output f of the 4 : 1 MUX shown in figure. is



(c) 
$$\overline{x} + \overline{y}$$
 (d)  $xy + \overline{x}$ 

Ans. (b)

Sol.

$$f = (\overline{x} \overline{y}.0 + \overline{x} y.1 + x \overline{y}.1 + x y.1)$$

$$= \overline{x} y + x \overline{y} + xy$$
  
k-map  $f$   $\overline{y}$   $y$   
 $\overline{x}$   $1$ 

**87.** The Boolean function A + BC is a reduced form of

(a) AB + BC (b) (c) A'B + AB'C (c)

(b) (A + B) (A + C) (d) (A +C)B

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



**GATE 2021** 

**Online Test Series** 

## CE ME EE ECE

- Matches level & orientation of GATE
- Thoroughly researched test papers
- Comprehensive analytical feedback
- Track & monitor your performance
- Get familiarised with GATE calculator
- Build upon hand-eye coordination
- 70 Tests

- **42** Topic-wise Tests
- **12** Subject-wise Tests
- **10** Mixed Subjects Tests
- 06 Mock Tests (Full Length)

**Registrations Open, Enrol Now** 

To register, visit iesmaster.org or contact IES MASTER help desk at 80100 09955, 97118 53908

| IES MASTER |  |
|------------|--|

Ans. (b)

f = A + BC

f = (A + B) (A + C)

of 10.23 V. The resolution is

Resolution =  $\frac{10.23}{20^{10}-1}$  = 10 mV

Option (a)  $xy + \overline{x}\overline{y} = \overline{x} \odot y$ 

Option (b)  $x \oplus \overline{y} = \overline{x} \overline{y} + x \overline{\overline{y}}$ 

 $= \overline{x} \overline{y} + xy = x \odot y$ 

 $= \mathbf{x} \odot \mathbf{y}$ 

Option (d) is false

propagation delay of (a) each flip-flop

(d) only circuit gates

(b) all flip-flop and gates

(c) flip-flops only with gates

Option (c)  $\overline{x} \oplus y = \overline{\overline{x}}y + \overline{x}\overline{y} = xy + \overline{x}\overline{y}$ 

Option (d)  $\overline{x} \oplus \overline{y} = \overline{\overline{x}}y + \overline{x}\overline{\overline{y}} = x\overline{y} + \overline{x}y$ 

A ripple counters speed is limited by the

A 10-bit D/A converter gives a maximum output

Which of the following expressions does NOT

(d)  $\overline{\mathbf{x}} \oplus \overline{\mathbf{y}}$ 

represent exclusive NOR of x and y?

(b) 20 mV

(d) 25 mV

(b) x⊕ <u>y</u>

= x⊕v

Using law

(a) 10 mV

(c) 15 mV

(a)  $xy + \overline{xy}$ 

(c) **x** ⊕ y

Sol.

88.

Ans.

Sol.

89.

Ans. (d)

Sol.

90.

Ans. (a)

(a)

|      | -        |         |          |            |         |
|------|----------|---------|----------|------------|---------|
| (a)  | Sampling | signals | less tha | in Nysuist | rate    |
| (b)  | Sampling | signals | more the | an Nyquis  | st rate |
| (c)  | Sampling | signals | equal to | o Nyquist  | rate    |
| ( 1) | o        |         |          |            |         |

91.

ES MASTER

Institute for Engineers (IES/GATE/PSUs)

(d) Sampling signals at a rate which is twice of Nyquist rate

#### Ans. (a)

92. Consider sinusoidal modulation in an AM system. Assuming no over modulation, the modulation index (μ) when the maximum and minimum values of the envelope, respectively are 3V and 1V is

When aliasing take place

Ans. (b)

Sol. 
$$\mu = \frac{V_{max} - V_{min}}{V_{max} + V_{min}}$$
$$= \frac{3-1}{3+1}$$
$$\mu = 0.5$$

**93.** The Q-factor of a waveguide resonator is given by  $(\omega_0 \text{ is resonant frequency, U} \text{ is energy}$ storage and  $\omega_L$  is power loss)

a) 
$$Q = \frac{\omega_0 U}{\omega_L}$$
 (b)  $Q = \frac{\omega_0 \omega_L}{U}$ 

(c) 
$$Q = \omega_0 U \omega_L$$
 (d)  $Q = \frac{U \omega_L}{\omega_0}$ 

Ans. (a)

Sol.

$$Q = \omega_0 \times \frac{\text{max. energy stored}}{\text{Power loss}}$$

$$Q = \frac{\omega_0 U}{\omega_1}$$

**94.** A speech signal is sampled at 8 kHz and encodes in PCM format using 8-bit/sample PCM data is transmitted through a baseband channel via 4-level PAM. Minimum Bandwidth required for transmission is

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



### **IES MASTER** Institute for Engineers (IES/GATE/PSUs)

UPPSC-AE-2020 Detailed Solution Electrical Engineering-II

|      | (a) 16 kHz   | (b) 8 kHz  |                      |
|------|--|--|----------------------|
|      | (c) 24 kHz   | (d) 10 kHz   |                      |
| Ans. | (a)  |  |                      |
| Sol. | Speech signal free   | uency of sampling  |                      |
|      | = 8 kHz = f <sub>s</sub>   |  |                      |
|      | No. of levels M =  | 4  |                      |
|      | No. of bits = $n = 8$  | 3 bits/sample  |                      |
|      | bit rate R <sub>b</sub> = nfs                                    |  |                      |
|      | $R_{b} = 8 \times$   | 8 = 64 kbps  |                      |
|      | Minimum bandwidt   | h = $\frac{R_b / 2}{\log_2 M} = \frac{64 / 2}{\log_2 4}$                               |                      |
|      | [B.W] <sub>min</sub> = 16 kHz                                    |  |                      |
| 95.  | For best low level X-band, an amplifi                            | noise performance in th<br>er should use   | ıe                   |
|      | (a) A bipolar trans  | istor  |                      |
|      | (b) a gunn diode   |  |                      |
|      | (c) A step recovery diode  |  |                      |
|      | (d) An IMPATT die  | ode  |                      |
| Ans. | (c)  |  |                      |
| 96.  | A lossless line of c<br>is terminated in pur<br>Standing Wave Ra | haracteristic impedance :<br>e reactance of -jz <sub>0</sub> , Voltag<br>tio (VSWR) is | z <sub>o</sub><br>je |
|      | (a) 10   | (b) 2  |                      |
|      | (c) 1  | (d) infinity   |                      |
| Ans. | (d)  |  |                      |
| Sol. | VSWR = $\frac{1+ R }{1- R }$                                     |  |                      |
|      | Here R = the refle   | ction coefficient  |                      |
|      | $R = \frac{Z_{L} - Z_{0}}{Z_{L} + Z_{0}} =$                      | $\frac{Z_{o} - jZ_{o}}{Z_{o} + jZ_{o}}$  |                      |
| 97.  | In colour TV receiv  | ver, varactor diode is use   | ed                   |
|      | (a) Deflection   | (b) Rectification  |                      |
|      | (c) Tuning   | (d) Both (a) and (b  | ))                   |
| Ans. | (c)  |  |                      |
|      |  |  |                      |

| 98. | FDM is an analog multiplexing technique used |
|-----|--|
|     | to combine                                   |

- (a) Analog signals
- (b) Digital signals
- (c) Both analog and digital signals
- (d) Alternatively passes analog and digital signal

#### Ans. (a)

- **99.** Large internal faults in transformer are protected by
  - (a) Merz-price percentage differential protection
  - (b) Mho and ohm relays
  - (c) Horn gaps and temperature relays
  - (d) Earth fault and positive sequence relays

#### Ans. (a)

**100.** If the fault current is 2000 A, the relay setting is 50% and CT ratio is 400 : 5, the PSM will be

- (a) 25 (b 15
- (c) 50 (d) 10
- Ans. (d)

9

$$PSM = \frac{2000}{400 \times 0.5}$$

PSM = 10

- 101. An ideal circuit breaker should offer
  - (a) Zero and infinite impedances before and after arc interruption respectively
  - (b) Infinity and zero impedances before and after arc interruption respectively
  - (c) Equal impednace before and after arc interruption
  - (d) None of these

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



#### Ans. (a)

**102.** A three-phase, 33 kV, oil circuit breaker is rated 1200 A, 2000 MVA, 3 sec. The symmetrical breaking current will be

| (a) 1200 A | (b) 3600 A   |
|------------|--------------|
| (c) 35 kA  | (d) 104.8 kA |

#### Ans. (c)

**Sol.** Breaking capacity =  $\sqrt{3}$  × rated voltage × symmetrical breaking current.

 $2000 = \sqrt{3} \times 33 \times$  symmetrical breaking current (in kA)

$$I_{BK} = \frac{2000}{\sqrt{3} \times 33}$$

 $I_{BK} = 35 \text{ kA}$ 

- **103.** With the help of reactive compensator, it is possible to have
  - (a) Constant voltage operation only
  - (b) Unity p.f. operation only
  - (c) Both constant voltage and unit p.f.
  - (d) Either constant voltage operation or unity p.f. operation.

#### Ans. (d)

- **104.** The most efficient torque producing actuating structure for the induction type relays
  - (a) Shaded pole structure
  - (b) Watt hour meter structure
  - (c) Induction cup structure
  - (d) Single induction loop structure

Ans. (c)

- **105.** Why are the ternary lead cables used near the railway track?
  - (a) Because they have high tensile strength
  - (b) Have a low coefficient of thermal expansion

- (c) Have low specific gravity
- (d) Can withstand shocks and vibrations

Ans. (c)

- **106.** Given that  $\frac{dy}{dx} = x^2 + y$ , with y(0) = 1, when x = 0, taking h = 0.2. The value of y after 1 iteration using Euler's modified method is
  - (a) 1.2 (b) 1.224
  - (c) 1.228 (d) 1.232

Ans. (\*)

Sol. 
$$y' = x^2 + y$$
;  $y(0) = 1$ ,  $x = 0$ ,  $h = 0.2$   
 $f(x, y) = x^2 + y$   
 $f(x_0, y_0) = f(0, 1) = 1$   
 $x_0 + \frac{1}{2}h = 0 + \frac{1}{2} \times 0.2 = 0.1$   
 $y_0 + \frac{1}{2}hf(x_0, y_0) = 1 + \frac{1}{2} \times 0.2 \times 1$   
 $= 1.1$ 

Modified Euler method.

$$y_{m+1} = y_m + hf\left(x_m + \frac{1}{2}h, y_m + \frac{1}{2}hf(x_m, y_m)\right)$$
  

$$m = 0,$$
  

$$y_1 = y_0 + hf\left(x_0 + \frac{1}{2}h, y_0 + \frac{1}{2}hf(x_0, y_0)\right)$$
  

$$= 1 + 0.2 \times f(0.1, 1.1)$$
  

$$= 1 + 0.2 (0.1^2 + 1.1)$$
  

$$\boxed{y_1 = 1.222}$$

- **107.** The points where Newton-Raphson method falls are called
  - (a) Floating
  - (b) Continuous
  - (c) Non-Stationary
  - (d) Stationary

Ans. (d)

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



- **Sol.** The point where the function f(x) approaches infinite are called as stationary points. At stationary points Newton Raphson fails.
- **108.** Newton-Raphson method is used to compute a root of the equation  $x^2 13 = 0$  with 3.5 as initial value. The approximation after one iteration is

| (a) 3.575 | (b) 3.676 |
|-----------|-----------|
| (a) 2 667 | (d) 2 607 |

- (c) 3.667 (d) 3.607
- Ans. (d)
- **Sol.** Given,  $f(x) = x^2 13 = 0$

As per Newton-Raphson method,

$$x_{1} = x_{0} - \frac{f(x_{0})}{f'(x_{1})} \quad \{:: f'(x) = 2x\}$$
$$x_{1} = 3.5 - \frac{(3.5)^{2} - 13}{2(3.5)}$$

$$x_1 = 3.607$$

So, the value after one iteration = 3.607

- **109.** Which one of the following materials is a diamagnetic material?
  - (a) Copper (b) Nickel
  - (c) Iron (d) Aluminium
- Ans. (a)
- **110.** The structure sensitive property of a super conductor is
  - (a) Critical magnetic field
  - (b) Transition temperature
  - (c) Critical current density
  - (d) None of the above
- Ans. (c)
- **111.** The 2's complement representation of decimal number [-17] is

- (a) [100110] (b) [101111] (c) [111110] (d) [110001]
- Ans. (b)

Sol.

[17] = 010001

$$[-17] = 110001$$
  
  $\uparrow$  (sign bit)

2's complement of [-17] = [1 0 1 1 1 1]

- **112.** The smallest integer that can be represented by an 8-bit number in 2's complement form is
  - (a) -256 (b) -128
  - (c) -127 (d) 0

#### Ans. (b)

Smallest integer =  $-2^{n-1} = -128$ 

- **113.** In a single phase induction motor, the reaction for having high resistance rotor is to achieve
  - (a) Reduced size
  - (b) Low starting torque
  - (c) High efficiency
  - (d) High aceleration

#### Ans. (d)

- **114.** BLDC motor is analogous to
  - (a) Permanent magnet synchronous motor
  - (b) DC motor
  - (c) Rotating transformer
  - (d) Single phase induction motor
- Ans. (d)
- **115.** In a squirrel cage rotor, the bars are NOT placed parallel to the shaft, but are skewed to have
  - (a) Greater mechanical strength
  - (b) Less rotor losses
  - (c) Uniform torque
  - (d) None of the above

Ans. (c)

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



# **SSC-JE** CEIMEIEE Mains Test Series

- Quality questions as per SSC-JE Mains exam syllabus and pattern
- Covers all technical topics as per SSC-JE Paper-II syllabus
- Designed to make students get into real exam mode
- Get the desired boost in confidence

Starts from 3 Jan

**1.5**<br/>Tests**11** Mixed Subjects Tests**4** Full Length Tests

**ENROLL NOW** 

F-126, Katwaria Sarai, New Delhi-110016 | Call +91 801 00 09955 Email: info@iesmaster.org



- **Sol.** Skewed by one slot pitch to reduce cogging torque, and this allows the motor to run quietly.
- 116. The presence of a dominant 7<sup>th</sup> harmonics in the winding distribution of 3-phase, 6-pole, 50 Hz, induction motor may cause the motor to crawl at a speed of about
  - (a) 750 rpm (b) 143 rpm
  - (c) 243 rpm (d) 500 rpm
- Ans. (b)
- Sol. Synchronous speed,

$$N_{\rm S} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

7<sup>th</sup> harmonics speed = 
$$\frac{N_S}{7} = \frac{1000}{7} \approx 143$$
 rpm

- **117.** A synchronous motor installed at the receiving end substation operates with such an excitation that it takes power at lagging power factor. Now if the applied voltage of the synchronous motor goes down, the power factor of synchronous motor will
  - (a) Remain constant
  - (b) Get down
  - (c) Be improved
  - (d) None of the above

Ans. (c)

- 118. Slip of an induction motor increases with
  - (a) Increase in current and decrease in torque
  - (b) Increase in current and torque
  - (c) Decrease in current and torque
  - (d) Decrease in current and increase in torque

Sol. I = 
$$\frac{V}{\left(\frac{R'_2}{S}\right)^2 + \left(X'_2\right)^2}$$

When slip increases means speed decreases, then supply current and torque increases.

- **119.** The slip of an induction motor normally does NOT depend on
  - (a) Rotor speed
  - (b) Synchronous speed
  - (c) Shaft torque
  - (d) Core-loss component

#### Ans. (d)

- Sol. Slip independent on core-loss component.
- **120.** A precise phase control for an A.C load can be controlled by a (an)
  - (a) Triac (b) SCR
  - (c) Transformer (d) Trigger pulse
- Ans. (a)
- **121.** UJT is known as
  - (a) Voltage controlled device
  - (b) Current controlled device
  - (c) Relaxation oscillator
  - (d) A transistor
- Ans. (c)
- **122.** In a step-up chopper, if V<sub>s</sub> is the source voltage and a is duty cycle, then the output voltage is
  - (a)  $V_{s}/(1+\alpha)$
  - (b)  $V_{s}(1+\alpha)$
  - (c)  $V_{s}(1-\alpha)$
  - (d)  $V_{s}/(1-\alpha)$

Ans. (d)

**Sol.** 
$$V_o = \frac{V_S}{1-\alpha}$$

**123.** A modern power semi-conductor device that combines the characteristics of both BJT and MOSFET

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org



| (a) | GTO  | (b) | FCT |
|-----|------|-----|-----|
| (C) | IGBT | (d) | MCT |

- Ans. (c)
- **124.** In a single phase full wave converter (M-2 connection) feeding a highly inductive load, the firing angle for each thyristor is a in the respective half cycle. This period of conduction of each thyristor is
  - (a)  $\pi a$  (b)  $\pi$
  - (c)  $\pi + a$  (d)  $\pi 2a$
- Ans. (b)
- **125.** In a 3-phase voltage source inverter used for speed control of induction motor anti parallel diodes are used across each switching device as shown in figure. The main purpose of diodes is to



**UPPSC-AE-2020** 

**Detailed Solution** 

**Electrical Engineering-II** 

Converter-2

- (a) Protect the switching device against over voltage
- (b) Provide the path for free wheeling current
- (c) Allow the motor to return energy during regeneration
- (d) Help in switching off the devices.

#### Ans. (c)

**Sol.** The main purpose of diodes is to allow the motor to return energy during regeneration.

F-126, Katwaria Sarai, New Delhi - 110 016 Ph: 011-41013406, Mobile: 8130909220, 9711853908 Web: www.iesmaster.org | E-mail: info@iesmaster.org